

Design of Analog Integrated Circuits

A/D AND D/A CONVERTERS

Piero Malcovati and **Franco Maloberti**

Department of Electronics

Integrated Microsystem Group

University of Pavia, 27100 Pavia, Italy

E-Mail: piero@ele.unipv.it, WWW: <http://ele.unipv.it/piero>

Tel. ++39-382-505205; Fax. ++39-0382-505677



University of Pavia

Integrated Microsystems Laboratory



OUTLINE

- **A/D Conversion Fundamentals**
- **A/D Converter Characteristics**
- **Nyquist-rate A/D Converters**
- **Oversampled A/D Converters**
- **D/A Converters**
- **Limits and Final Considerations**



A/D CONVERSION FUNDAMENTALS

- A/D converters accomplish two key operations: **sampling** and **quantization**

- **Sampling** $\rightarrow x^*(nT_s) = \sum_{n=-\infty}^{\infty} x(t)\delta(t - nT_s)$

- The output of an ideal sampler is a series of delta functions weighted by the input **$x(nT)$**

- The spectrum of the sampled signal x^* is


$$X^*(s) = \sum_{n=-\infty}^{\infty} x(nT_s)e^{-snT_s} = \frac{1}{T_s} \sum_{n=-\infty}^{\infty} X(s - jn\omega_s)$$



A/D CONVERSION FUNDAMENTALS

□ $X(s)$ is the spectrum of the continuous-time signal $x(t)$

↳ **Aliasing** → Anti-aliasing filter

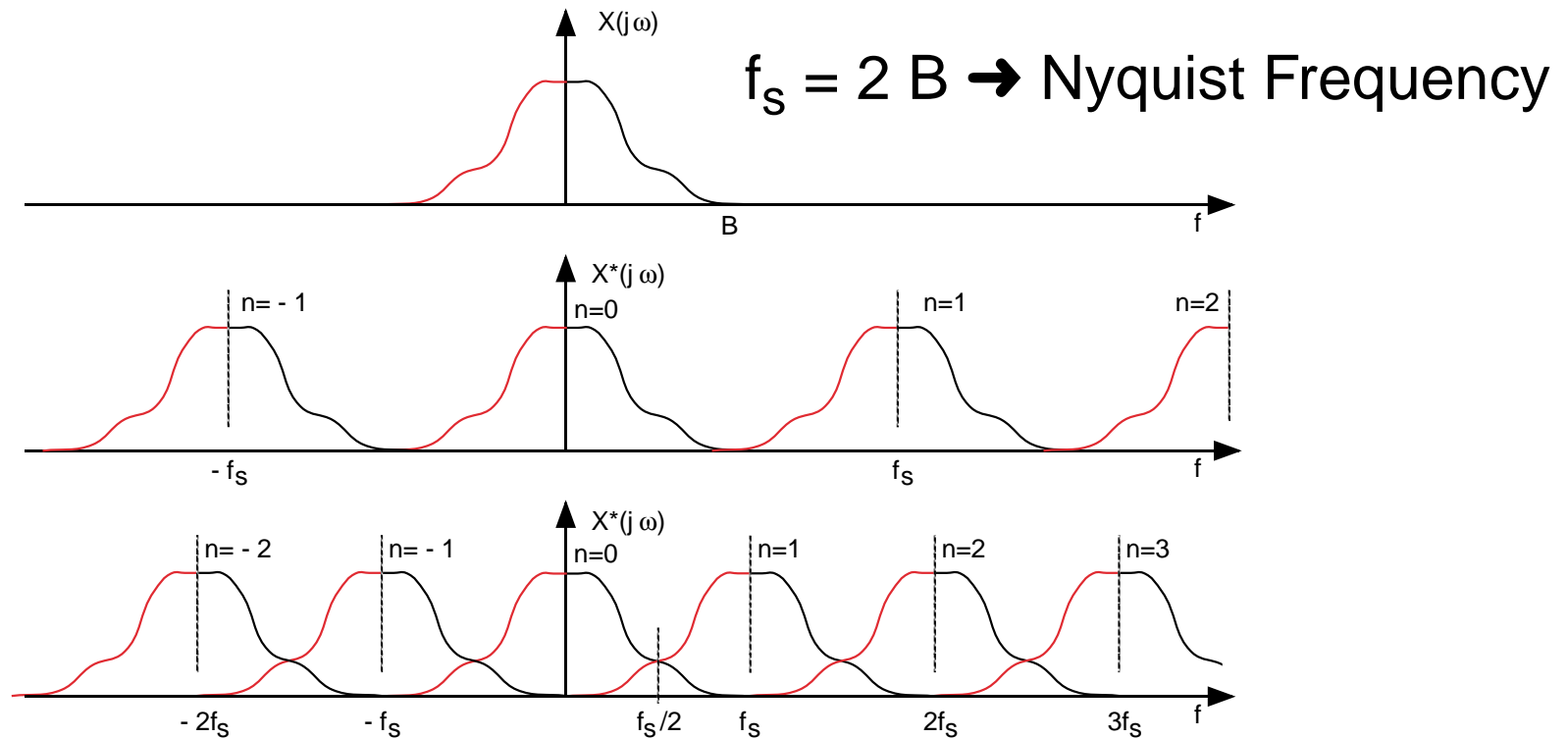

A/D CONVERSION FUNDAMENTALS

- ❑ **Quantization** → The number of bits N of the digital code is **finite**
 - ↳ N -bits → 2^N codes, each code represents a **quantization level**
- ❑ The amplitude of the constant spacing between quantization levels is $\Delta = V_{fs} / 2^N$ (where V_{fs} is the **full-scale amplitude** and Δ is the **quantization step**)
 - ↳ For example, a 10-bit converter with full-scale amplitude equal to **1.023 V** encodes the analog input with **1 mV** discretization
 - ↳ If the input voltage is **624.8 mV**, the digital output corresponds to the closer quantization level → **624.5 mV**
 - ↳ Since the quantization level is not equal to the input voltage, an error affects the output (**0.3 mV** in the example)





A/D CONVERSION FUNDAMENTALS

- ❑ The error due to the quantization process is called **quantization error** $\varepsilon_Q \rightarrow -\Delta / 2 < \varepsilon_Q < \Delta / 2$
- ❑ The quantization error represent an **inherent limit** of any data converter \rightarrow The quantization error is zero only if the number of bits of the digital code is infinite
- ❑ The quantization error is a consequence (and a measure) of the finite **A/D converter resolution**
- ❑ In an analog system the dynamic range performance is measured by the **Signal-to-Noise Ratio (SNR)** \rightarrow It is useful to define the converter resolution in terms of **SNR** (in addition to the number of bits)



IS QUANTIZATION ERROR NOISE?

 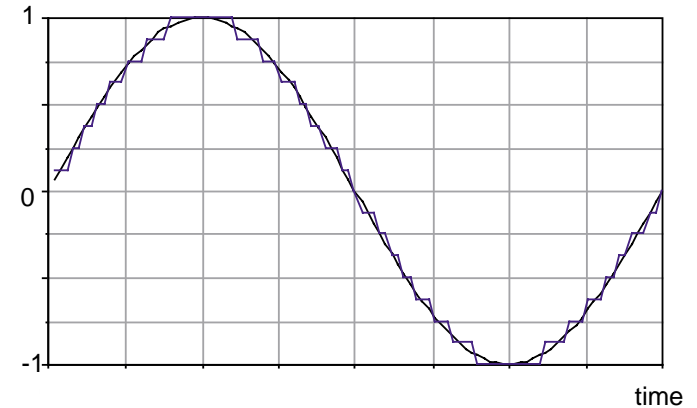
- ❑ **Quantization error** can be considered a **noise** if
 - ➔ All quantization levels occur with equal probability
 - ➔ The quantization steps are uniform
 - ➔ The quantization error is not correlated with the input signal
 - ➔ A large number of quantization levels are used
- ❑ In many practical situations the above rules are **not strictly fulfilled** (for example Sigma-Delta Modulators)



FEATURES OF THE QUANTIZATION NOISE

- The **quantization error** is limited to the interval $-\Delta / 2 < \varepsilon_Q < \Delta / 2$
 - ↳ The **probability distribution function** of ε_Q , $p(\varepsilon_Q)$, is assumed constant
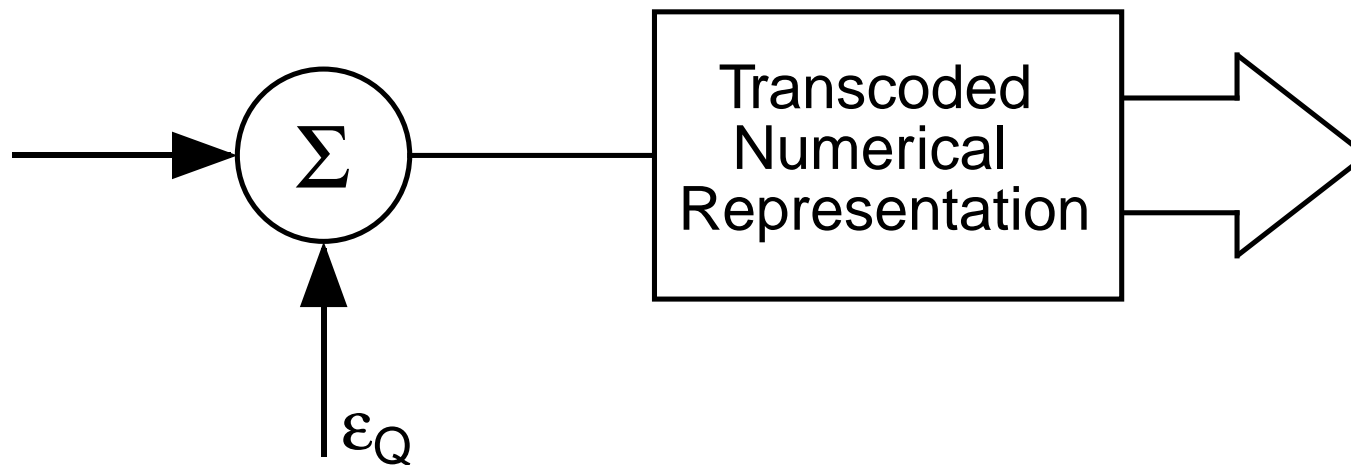
$$p(\varepsilon_Q) = \frac{1}{\Delta} \text{ for } \varepsilon_Q \in \left[-\frac{\Delta}{2}, \frac{\Delta}{2}\right]; \quad p(\varepsilon_Q) = 0 \text{ otherwise}$$



FEATURES OF THE QUANTIZATION NOISE

- **Power** → The **power** for the quantization noise P_Q is

$$P_Q = \int_{-\infty}^{\infty} \varepsilon_Q^2 p(\varepsilon_Q) d\varepsilon_Q = \int_{-\frac{\Delta}{2}}^{\frac{\Delta}{2}} \frac{\varepsilon_Q^2}{\Delta} d\varepsilon_Q = \frac{\Delta^2}{12}$$

- **Sine wave** with amplitude $V_{fs} / 2$ → Power $V_{fs}^2 / 8$

$$\text{SNR} = 10 \text{Log} \frac{P_{\text{sig}}}{P_{\varepsilon_Q}} = \frac{V_{fs}^2 / 8}{[V_{fs} / (2^N - 1)]^2 / 12} \cong 6.02N + 1.76 \text{ [dB]}$$



FEATURES OF THE QUANTIZATION NOISE

- **Triangular wave** with amplitude $V_{fs} / 2 \rightarrow$ Power $V_{fs}^2 / 12$

$$\text{SNR} = \frac{V_{fs}^2 / 12}{[V_{fs} / (2^N - 1)]^2 / 12} \cong 6.02N \quad [\text{dB}]$$

- **Effective number of bits N_{eff}**

$$N_{\text{eff, sin}} = \frac{\text{SNR}_{\text{dB}} - 1.76}{6.02}$$

$$N_{\text{eff, tr}} = \frac{\text{SNR}_{\text{dB}}}{6.02}$$



FEATURES OF THE QUANTIZATION NOISE

- Power spectrum → Shows in which way the noise power is **distributed** over the Nyquist interval

- ↳ The power spectrum is the Laplace transform of the **autocorrelation function** $R_\varepsilon(\tau)$ of ε_Q


$$P_\varepsilon(f) = \int_{-\infty}^{\infty} R_\varepsilon(\tau) e^{-j2\pi f\tau} d\tau$$

- The **autocorrelation function** of the noise is difficult to express
 - ↳ Successive quantization error samples are **weakly correlated**
 - ↳ The autocorrelation $R_\varepsilon(\tau)$ almost vanishes for $-T_s > \tau > T_s$




FEATURES OF THE QUANTIZATION NOISE

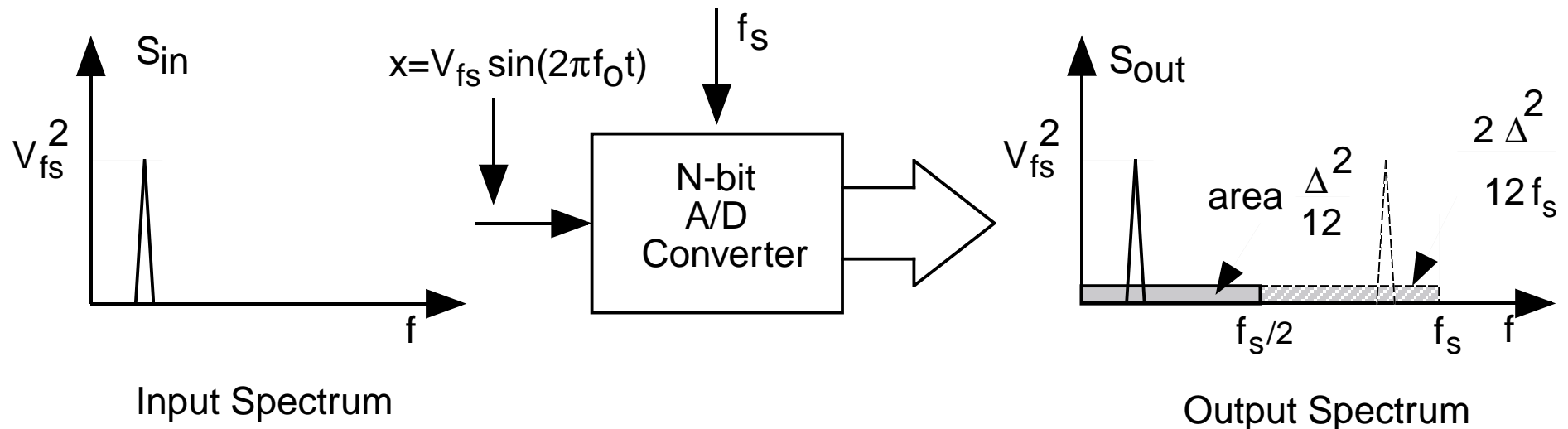- The quantization noise is an **additive white noise**
 - ↳ **Power** $\rightarrow \Delta^2 / 12$, uniformly spread over the Nyquist band
 - ↳ **Power spectral density** $\rightarrow 2 \Delta^2 / 12 f_s$




A/D CONVERTER ARCHITECTURES

 - Different **A/D converter** architectures either Nyquist rate and oversampled
 - ↳ **Trade-off** between speed and resolution
 - ↳ **Application** dependent



NYQUIST RATE VS OVERSAMPLED CONVERTERS

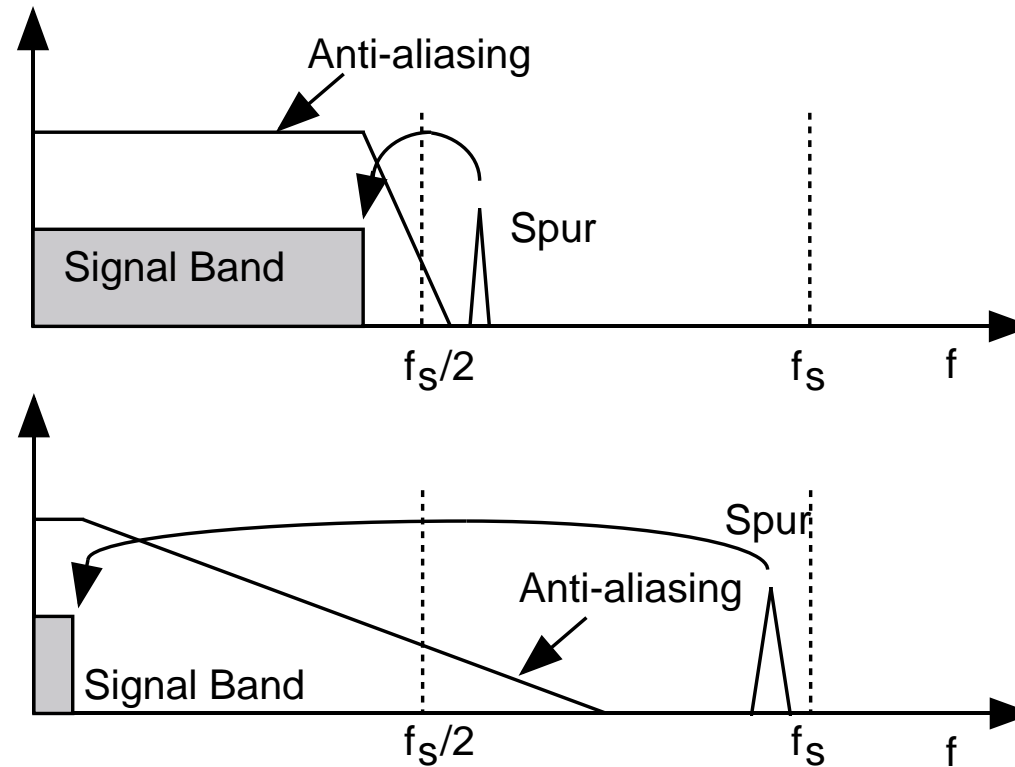- ❑ **Anti-aliasing filter** → Significantly attenuate spurs while preserving the signal band






NYQUIST RATE VS OVERSAMPLED CONVERTERS

- ❑ In Nyquist rate converters the signal band occupies almost the **entire Nyquist interval** → The **entire quantization noise power** affects the signal
- ❑ In oversampled converters the signal band occupies only a **fraction of the Nyquist interval** → Only **part of the quantization noise power** affects the signal
- ❑ The SNR can be improved by **filtering** in the digital domain the **out-of-band quantization noise**
- ❑ The **cost** that we have to pay is an additional **digital filter** and analog operation at **high speed**



ADVANTAGES OF OVERSAMPLING

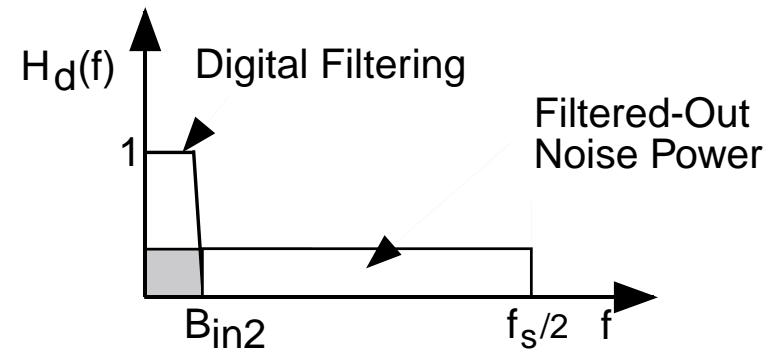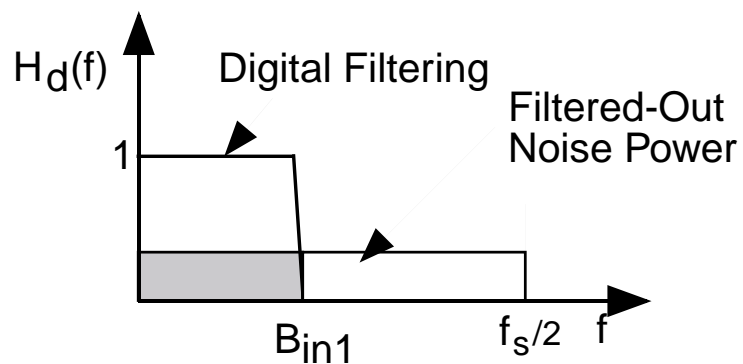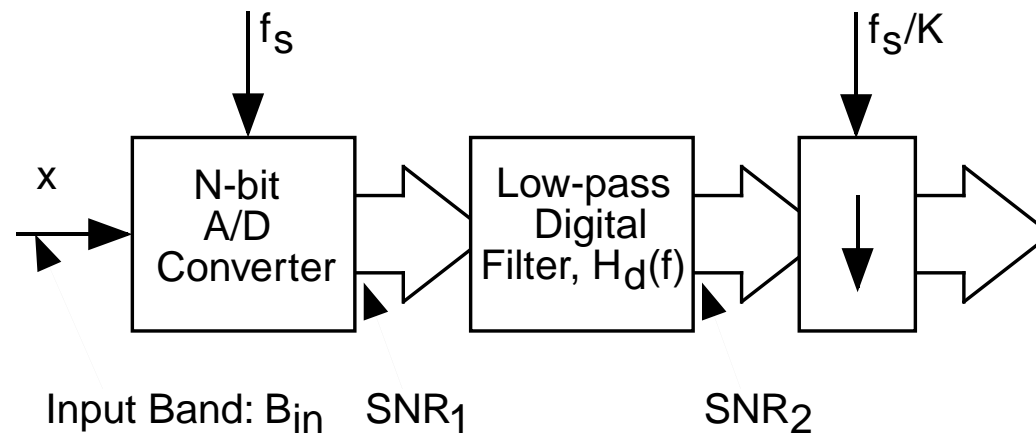- ❑ Oversampling trades **speed** with **resolution**



ADVANTAGES OF OVERSAMPLING

- ❑ **Doubling** the sampling frequency (oversampling) → The in band noise power becomes **half**
 - 😊 **SNR** grows by 3 dB
 - 😊 The **effective number of bits** increases by 0.5
 - 😞 For gaining **one bit** of resolution it is necessary to increase the sampling by a factor **4**
 - 😞 For increasing the resolution, for example, by **5 bits** the sampling frequency should be multiplied by **1024!**
- ❑ **Oversampling** by itself is not a convenient technique for enhancing resolution → To achieve substantial benefits, we have to use also **noise shaping**




A/D CONVERTER CHARACTERISTICS

- ❑ The key features characterizing an A/D converter are **speed** and **accuracy**
- ❑ The **conversion rate** quantifies the speed → It is measured in Hertz or in samples per second (S/s)
- ❑ The **number of bits** or the **SNR** (expressed in dB) are the parameters normally used to quantify the accuracy or the resolution
- ❑ Alternatively, accuracy can be expressed as a **fraction of the full-scale** signal → It is expressed in parts-per-million (ppm)
- ❑ Many effects influence both the **dynamic** and the **static** behavior



SPEED CHARACTERISTICS

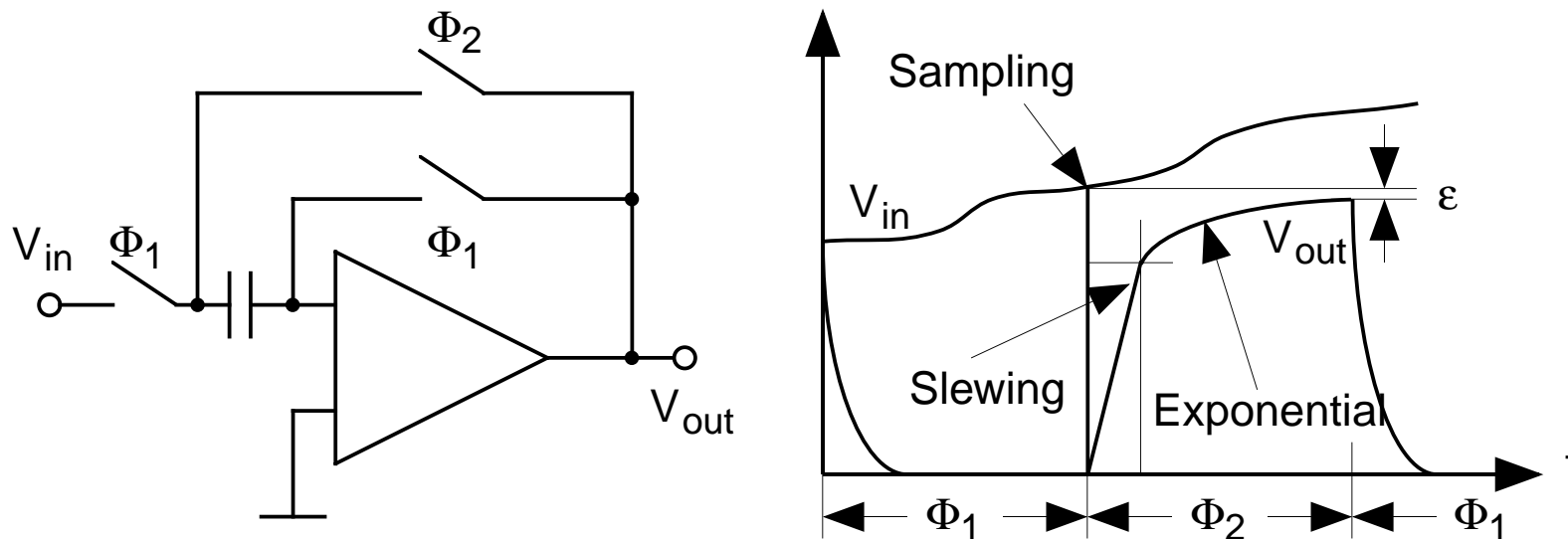- ❑ The **maximum sampling rate** achieved by a converter is related to the time required for completing the specific processing functions
- ❑ **Example** → Sample and hold with real operational amplifier



SLEW RATE AND BANDWIDTH

- The **non-linear** response results from the following equations

$$\rightarrow \begin{cases} V_{\text{out}}(t) = \text{SR}t & \text{for } t \leq t_{\text{sl}} \\ V_{\text{out}}(t_{\text{sl}}) = \text{SR} \cdot t_{\text{sl}} = V_{\text{in}} - V_{\text{lin}} & \text{for } t = t_{\text{sl}} \\ V_{\text{out}}(t) = (V_{\text{in}} - V_{\text{lin}})e^{-(t-t_{\text{sl}})\tau} & \text{for } t > t_{\text{sl}} \end{cases}$$

→ SR → **slew-rate**, V_{lin} → **linear range**, τ → **time constant** (bandwidth) and T_S → **sampling period**

- The **slewing time** must be a small fraction of T_S
- The **bandwidth** of the amplifier must be high enough to allow a suitable number of time constants for the exponential settling




CLOCK JITTER

- ❑ Sampling **clock jitter** → If the command used for opening the sampling switch is affected by jitter, the **sampling is not uniform**
- ❑ The effect can be described as a **noise source** → **Jitter noise** ε_{ji}
- ❑ The effect of ε_{ji} can be estimated by considering the sampling of a sinusoidal signal
$$\varepsilon_{ji} = A \{ \sin[\omega_{in}(nT + \delta_{ji})] - \sin[\omega_{in}nT] \} = \delta_{ji} A \omega_{in} \cos(\omega_{in}nT)$$
- ❑ The error is relevant when the associated **power** $(A \delta_{ji} \omega_{in})^2 / 8$ becomes comparable to the **quantization noise**
- ❑ The limit is achieved when $(\delta_{ji} \omega_{in})^{-2}$ approaches the **SNR**



APERTURE DISTORTION

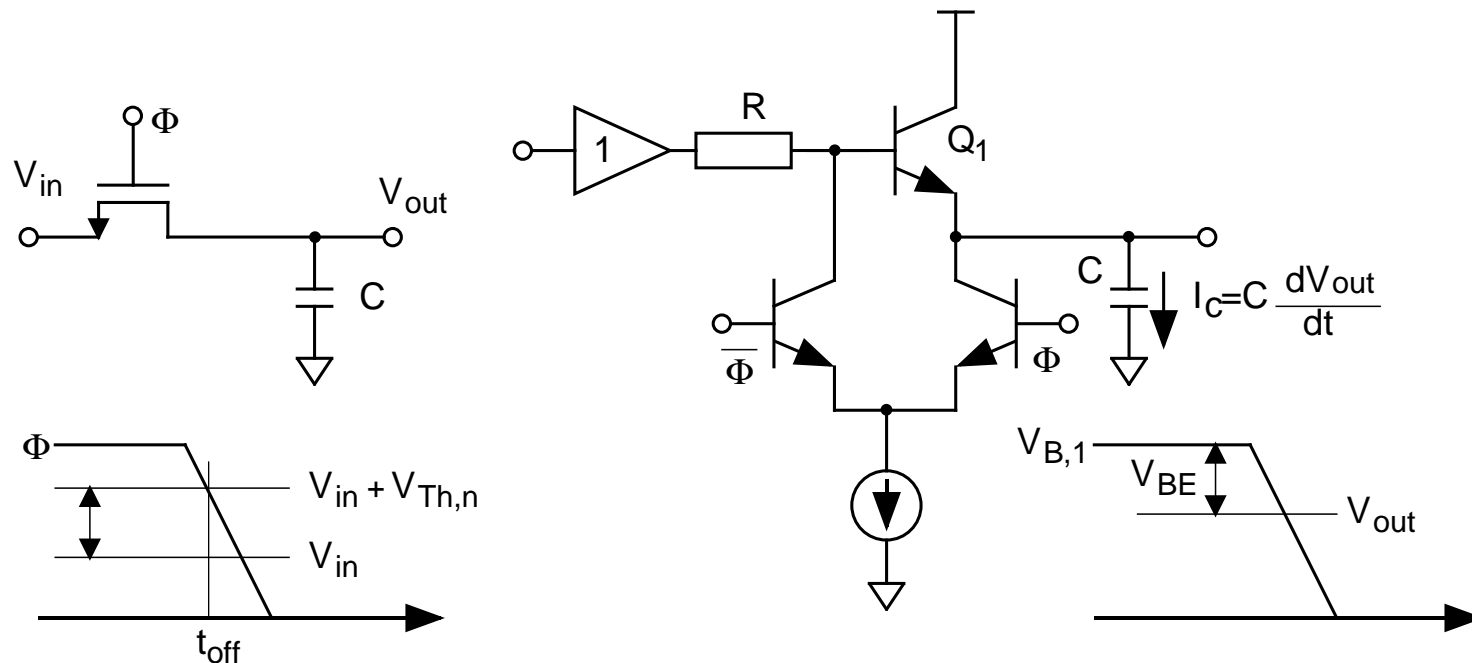- Aperture distortion → The **sampling instants** depends on the **input amplitude** since the exact instant of sampling occurs when the switch disconnects the input from the storing element



APERTURE DISTORTION

- ❑ The **aperture distortion** describes the dependence of the sampling instants on the input amplitude
- ❑ At **very high frequency** the use of **MOS** switches becomes problematic when also high resolution is required
 - ➔ The finite **on-resistance** of the switch R_{on} and the **sampling capacitor** C lead to a time constant that affects the tracking of the input
 - ➔ $R_{on} = L / [W C_{ox} \mu (V_{GS} - V_{Th} - V_{DS})]$
 - ➔ The on-resistance of a **minimum area** n-channel transistor operating with **1 V overdrive** and a negligible V_{DS} is as high as **10 k Ω** ($t_{ox} = 15$ nm, $\mu_n = 520$ cm² / V s) → With a sampling capacitance of 1 pF the time constant becomes 10 ns








RESOLUTION CHARACTERISTICS

- ❑ An A/D converter **never** reaches the theoretical **SNR** corresponding to the desired **number of bits**
 - ↳ Various **static** or **dynamic** errors determine extra noise that, in turn, deteriorates the **output accuracy**
- ❑ Imperfections affecting the **static behavior**
 - ↳ The input-output **transfer characteristic** represents the **digital** output code as a function of the **analog** input signal
 - ↳ Ideally the input-output transfer characteristic of an A/D converter is a **2^N step staircase** with uniform step amplitude
 - ↳ Errors in the transfer characteristic → **Offset** error, **gain** error, **monotonicity** error, **missing code** error, **differential linearity** error, **integral linearity** error




STATIC ERRORS

  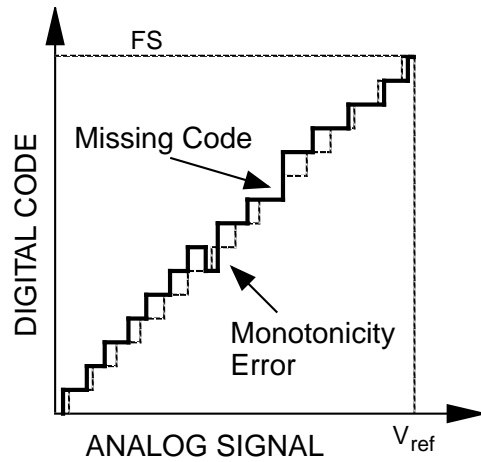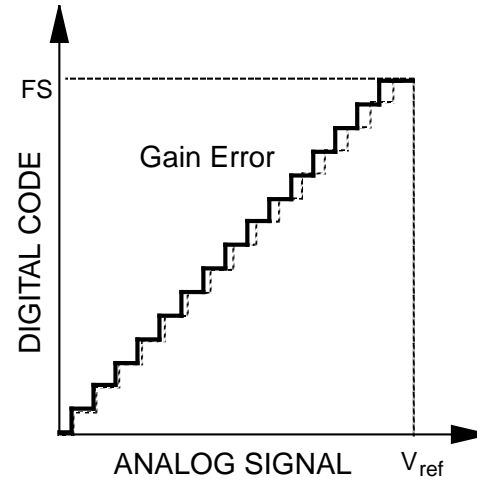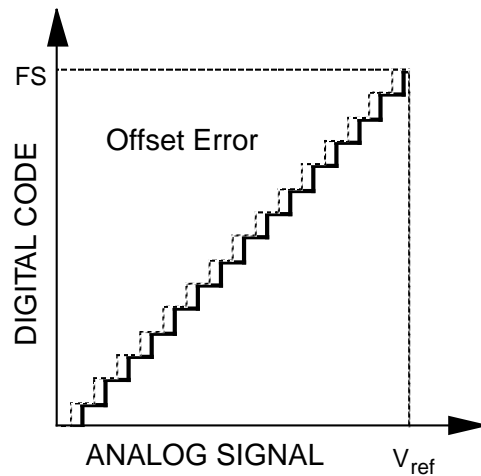

NON LINEARITY ERRORS

 - The **integral non-linearity** represents a distortion of the input-output transfer characteristic and leads to **harmonic distortion**, degrading the **spurious free dynamic range**



NYQUIST RATE A/D CONVERTERS

- ❑ High speed and low-resolution A/D converters
- ❑ The sampling frequency used in Nyquist-rate converters is close to the highest possible limit allowed by the technology
- ❑ The trend in signal processing systems is to place A/D converters as close as possible to the analog input
 - ➔ Most of the processing is performed in the digital domain
 - 😊 Advantage → Flexibility (the system can be reconfigured just by changing the software)
 - ☹ Problem → Large band systems (telecommunications) require both high speed of operation and high resolution




NYQUIST RATE ARCHITECTURES

- Full flash A/D converters
- Two-step flash A/D converters
- Folding A/D converters
- Successive approximation A/D converters
- Interleaved A/D converters
- Pipeline A/D converters




FULL FLASH A/D CONVERTERS

 - ❑ Thermometric coding
- ❑ Resistive string to achieve the quantization voltages required
- ❑ An N -bit converter requires
 - ↳ 2^N series resistors
 - ↳ $2^N - 1$ comparators
- ❑ Conversion time → One clock cycle



FULL FLASH A/D CONVERTERS

 - Limits to **accuracy**
 - ☹ **Matching** between integrated resistors
 - ☹ Comparator **offset**
 - ☹ **Loading impedance** of each tap of the resistive string




FULL FLASH A/D CONVERTERS

- ❑ An inherent **limitation** of the full flash architecture comes from the **exhaustive approach** used
- ❑ N bit of resolution require $2^N - 1$ comparators
 - ☹ The complexity of the circuit increases **exponentially** with the **number of bits** and the chip **area** and the **power** consumption become unacceptable
 - ☹ The **load at the input terminal** increases exponentially with the number of bits
- ❑ Suitable for **very high speed, low resolution** A/D converters (for example for video applications)



TWO-STEP FLASH A/D CONVERTERS

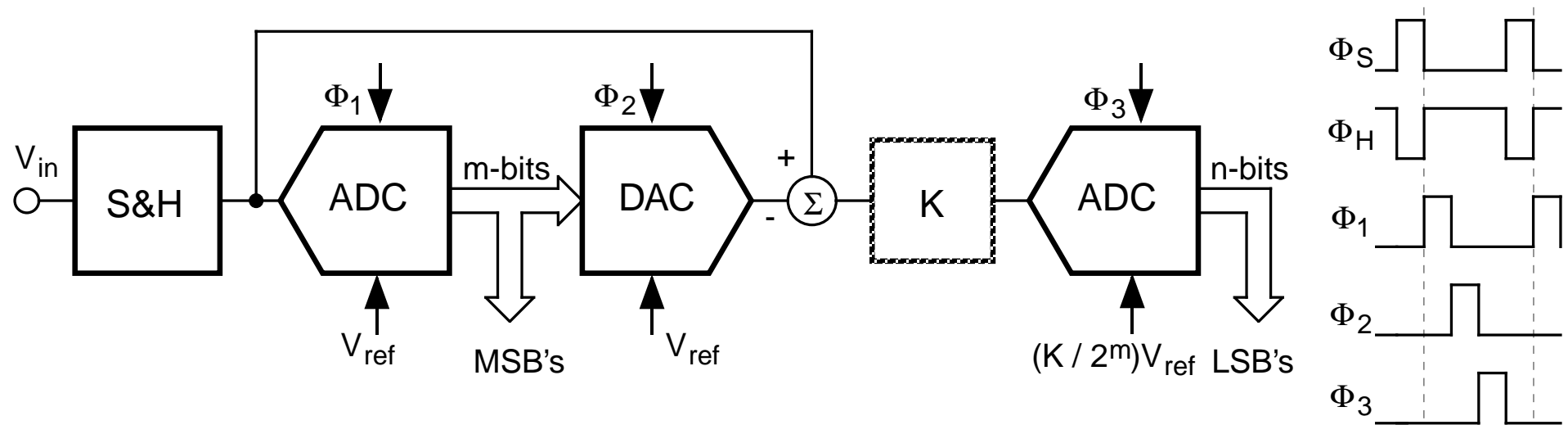- ❑ The advantage of the **full flash** method vanishes when the **number of bits** exceeds **8** or **9**
- ❑ **Two-step flash** A/D converter → **Coarse** conversion followed by a **fine** conversion



TWO-STEP FLASH A/D CONVERTERS

- ❑ The achieved **resolution** is $N = m + n$
- ❑ If the **subtraction** and the **amplification** by the factor K do not require additional clock cycles, the **conversion time** is two clock cycles
- ❑ The **two-step flash** architecture requires two full flash **A/D converters**, a **D/A converter** and a **subtracting amplifier**
- ❑ The number of **comparators** required is significantly **reduced** with respect to the full flash architecture → Only $(2^m + 2^n - 2)$ instead of 2^{n+m}



TWO-STEP FLASH A/D CONVERTERS


- ❑ Two-step flash A/D converter **limitations**
 - ☹ The **subtracting amplifier** can be the real limit to **speed**, since subtraction and amplification must settle within half of a quantization step, thus requiring time
 - ☹ **Successive samples** are weakly **correlated** → The subtracting amplifier must ensure **large output swing** within the subtracting period
 - ☹ Typically an **additional clock cycle** for the subtraction and amplification operation is required
 - ☹ The **mismatch** between the coarse and fine **reference voltages** or an error in the multiplying factor degrade the linearity



TWO-STEP FLASH A/D CONVERTERS

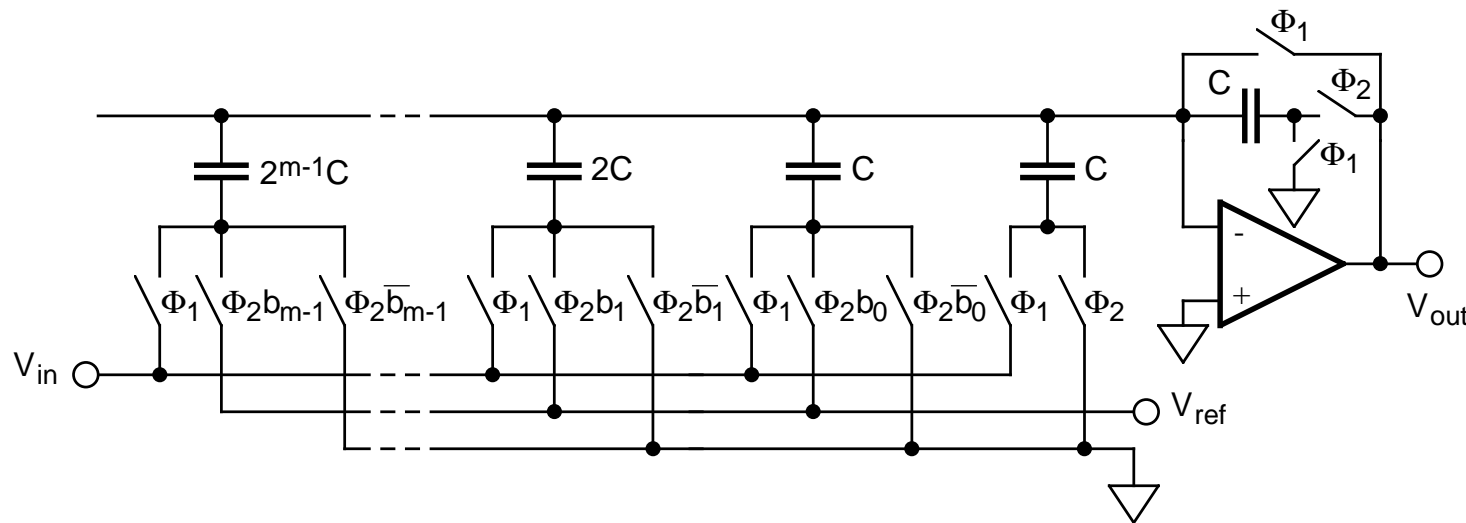- Example → Switched capacitor circuit which incorporates DAC, subtractor and multiplier by a factor 2^m ($B = b_{m-1}, \dots, b_0$)

$$V_{\text{out}} = 2^m V_{\text{in}} - \sum_{i=0}^{m-1} V_{\text{ref}} 2^i b_i = 2^m \left[V_{\text{in}} - V_{\text{ref}} \frac{B}{2^m} \right]$$




FOLDING A/D CONVERTERS

- The **folding** technique is based on a **non-linear preprocessing** of the input signal before the A/D conversion


$$V_{\text{out}} = V_{\text{in}} - \frac{j}{k} V_{\text{ref}} \quad \text{for } \frac{j}{k} V_{\text{ref}} < V_{\text{in}} \leq \frac{j+1}{k} V_{\text{ref}}, j \text{ even}$$
 
$$V_{\text{out}} = \frac{j+1}{k} V_{\text{ref}} - V_{\text{in}} \quad \text{for } \frac{j}{k} V_{\text{ref}} < V_{\text{in}} \leq \frac{j+1}{k} V_{\text{ref}}, j \text{ odd}$$





BIPOLAR FOLDING A/D CONVERTERS
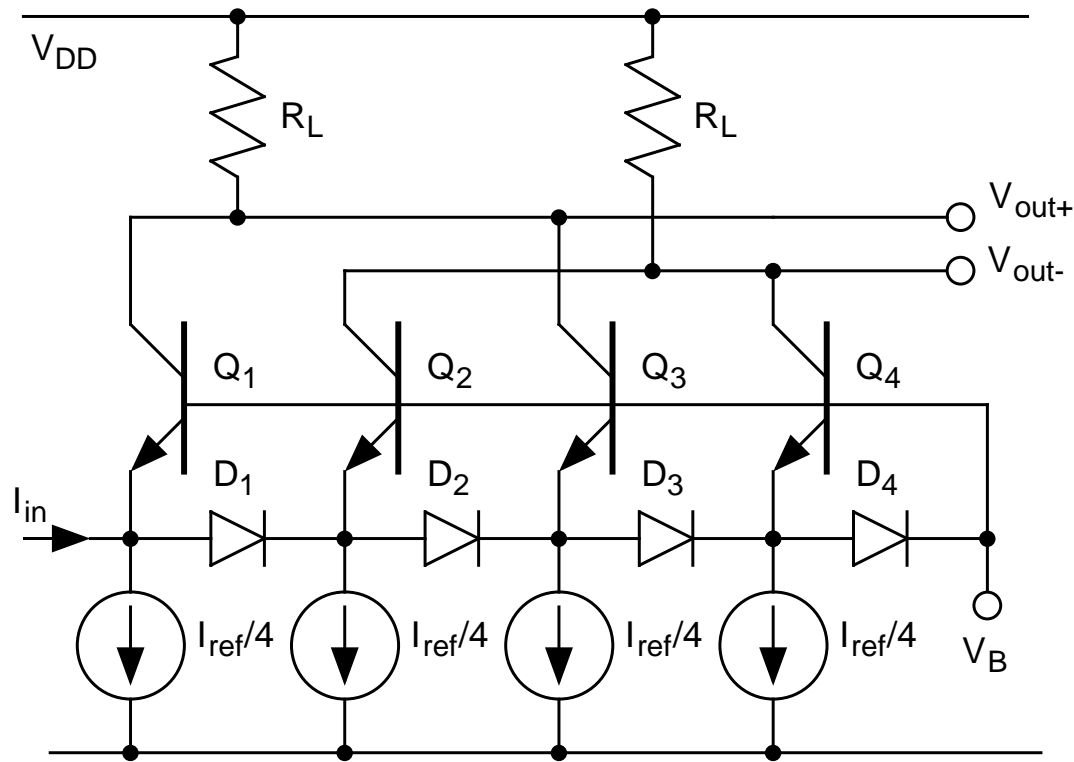
$$I_{in} < \frac{I_{ref}}{4} \begin{cases} V_{out+} = V_{DD} - R_L I_{ref}/2 + R_L I_{in} \\ V_{out-} = V_{DD} - R_L I_{ref}/2 \end{cases} \quad I_{in} < \frac{I_{ref}}{2} \begin{cases} V_{out+} = V_{DD} - R_L I_{ref}/4 \\ V_{out-} = V_{DD} - R_L I_{ref}/2 + R_L I_{in} \end{cases}$$




CMOS FOLDING A/D CONVERTERS

 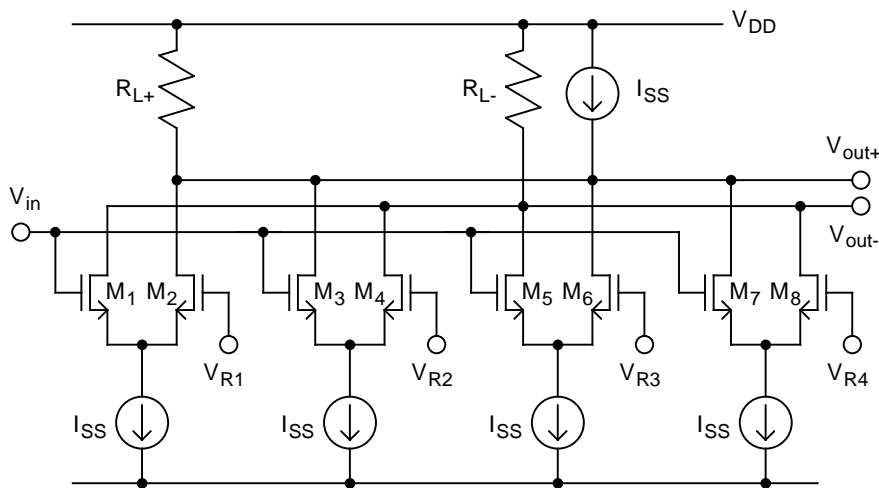- The **linear region** of the input-output transfer characteristic depends on the **overdrive voltage** of the differential pairs
 - ☹ **Smaller** overdrive → Steeper slope and wider corners
 - ☹ **Larger** overdrive → Full swing not achievable
- The **gain** depends on the $g_m R_L$ product



DOUBLE-FOLDING A/D CONVERTERS

 - ❑ **Rounding** in the transitions between **segments** → Significant **error** in a wide range near the **segment margins**





FOLDING A/D CONVERTERS

- ❑ The **current gain** β of bipolar transistors, the **matching** between MOS transistors, the **inaccuracy** of current sources and the **mismatch** of load resistances influence the **precision**
- ❑ Typical values of β and typical matching performances in integrated technology lead to an **error** of the range of **0.1%**
 - ↳ Maximum **resolution** is 10 bit
- ❑ **Speed** of **bipolar** implementations → More than 100 MHz
- ❑ **Speed** of **CMOS** implementations → Depends on the feature size of the technology




INTERPOLATING A/D CONVERTERS

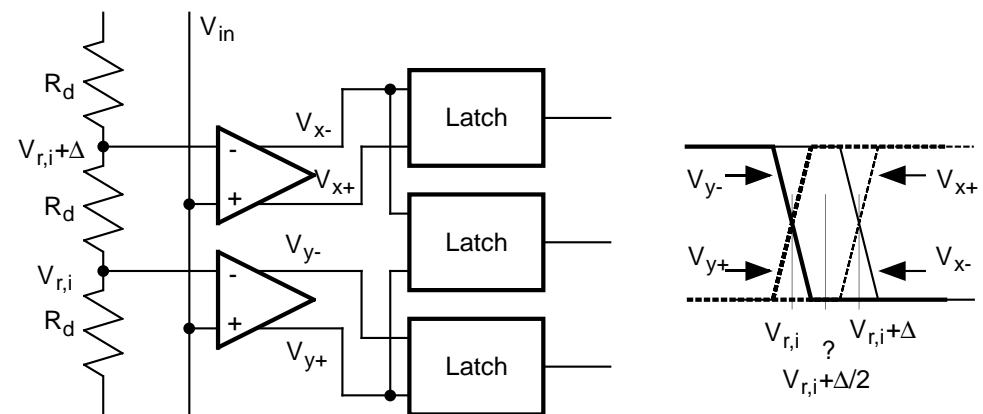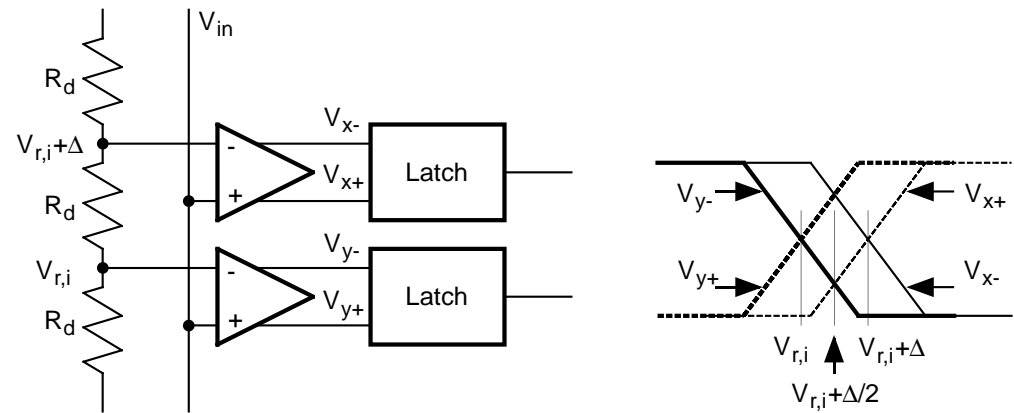- ❑ **Interpolation** → Reduced complexity
- ❑ The **interpolation** technique can be applied in the situations where **two analog signals** can be used to determine the **same digital code**
- ❑ The **interpolation** technique allows us to extract one or more **additional codes**




FOLDING-INTERPOLATING A/D CONVERTERS

 

SUCCESSIVE APPROXIMATION A/D CONVERTERS

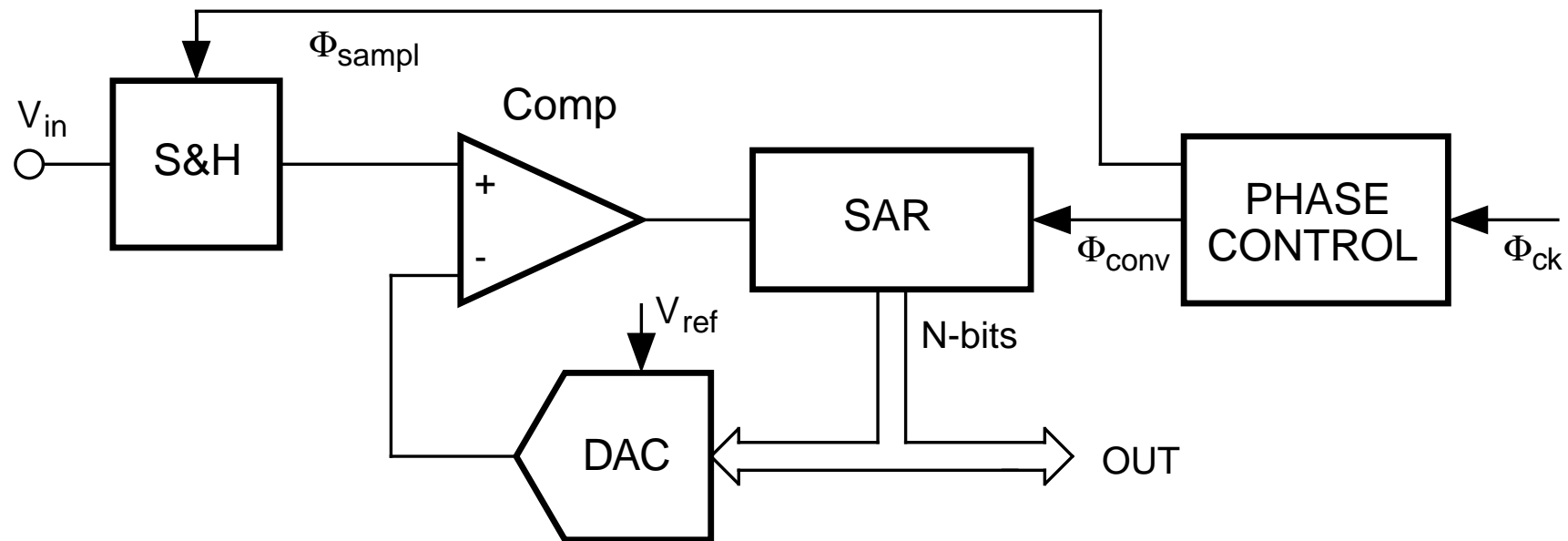- ❑ **Successive approximation** A/D converters → Optimal solution for **medium speed** and **moderate accuracy** (10-12 bit)
- ❑ **Conversion time** for N bits of resolution → N + 1 clock cycles (one clock cycle is required for sampling the input signal)



SUCCESSIVE APPROXIMATION A/D CONVERTERS

- ❑ The **Sample and Hold** (S&H) block samples the input signal at the beginning of each conversion cycle
- ❑ A **Successive Approximation Register** (SAR) controls the **Digital-to-Analog Converter** (DAC) which generates the proper sequence of approximations
- ❑ The **Comparator** (Comp) compares the approximations generated by the DAC with the output of the S&H and determines one bit of the digital output in each clock period
- ❑ The logic used is based on the **binary search** starting from the **Most Significant Bit** (MSB)



SUCCESSIVE APPROXIMATION A/D CONVERTERS

- **Principle of operation** → The digital representation **B** ($b_{N-1}, b_{N-2}, \dots, b_0$) of an analog signal V_{in} is

$$V_{in} = \frac{V_{ref}}{2} b_{N-1} + \frac{V_{ref}}{2^2} b_{N-2} + \dots + \frac{V_{ref}}{2^N} b_0 + \frac{V_{ref}}{2^{N+1}} + \varepsilon_Q$$


- ↳ $V_{ref} / 2^{N+1}$ → **1/2 LSB shift** of the transfer characteristic
- ↳ ε_Q → **Quantization error**

- The **MSB** b_{N-1} is determined with a comparison between V_{in} and $V_{ref} / 2$
- The next bit b_{N-2} is determined with a comparison between V_{in} and $b_{N-1} V_{ref} / 2 + V_{ref} / 4$




SUCCESSIVE APPROXIMATION REGISTER

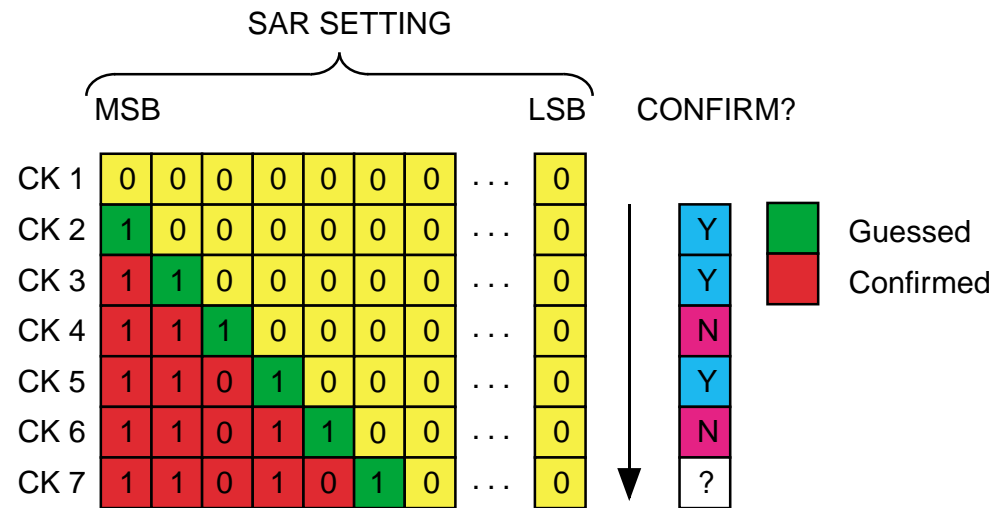- Successive approximation register (SAR) → Control of the DAC
 - ↳ Sampling of the input → CK 1
 - ↳ The conversion cycle starts at CK 2 → MSB = 1, LSBs = 0
 - ↳ The decision of the comparator successively determines the value of the bits



SUCCESSIVE APPROXIMATION A/D CONVERTERS

 - ❑ Charge redistribution A/D converter
 - 😊 The comparator operates **referred to ground** instead of processing the output of the DAC and the sampled input



SUCCESSIVE APPROXIMATION A/D CONVERTERS


- ❑ During the **first clock period** the circuit samples the input
- ❑ The **total charge** stored on the capacitive array is
$$Q_{\text{tot}} = 2^N C (V_{\text{in}} - V_{\text{os}})$$
- ❑ **Sampling period** → The operational amplifier is **buffer connected**
- ❑ **Conversion cycle** → The operational amplifier is used in **open loop** as a **comparator**
- ❑ After the **determination** of the MSB, the voltage at the inverting input of the comparator becomes

$$V_x = \frac{2^{N-1} C}{C_{\text{tot}}} V_{\text{ref}} - (V_{\text{in}} - V_{\text{os}}) = \frac{1}{2} V_{\text{ref}} - V_{\text{in}} + V_{\text{os}}$$




SUCCESSIVE APPROXIMATION A/D CONVERTERS

 - ❑ Charge on capacitor $2^{N-1} C \rightarrow Q_{C_{N-1}} = 2^{N-1} C \left(\frac{V_{\text{ref}}}{2} + V_{\text{in}} - V_{\text{os}} \right)$
- ❑ The **total charge** on the top plate is unchanged \rightarrow The remaining charge is **distributed** in the rest of the capacitive array
- ❑ **Drawback** \rightarrow **Overdrive recovery** of the comparator



INTERLEAVED A/D CONVERTERS

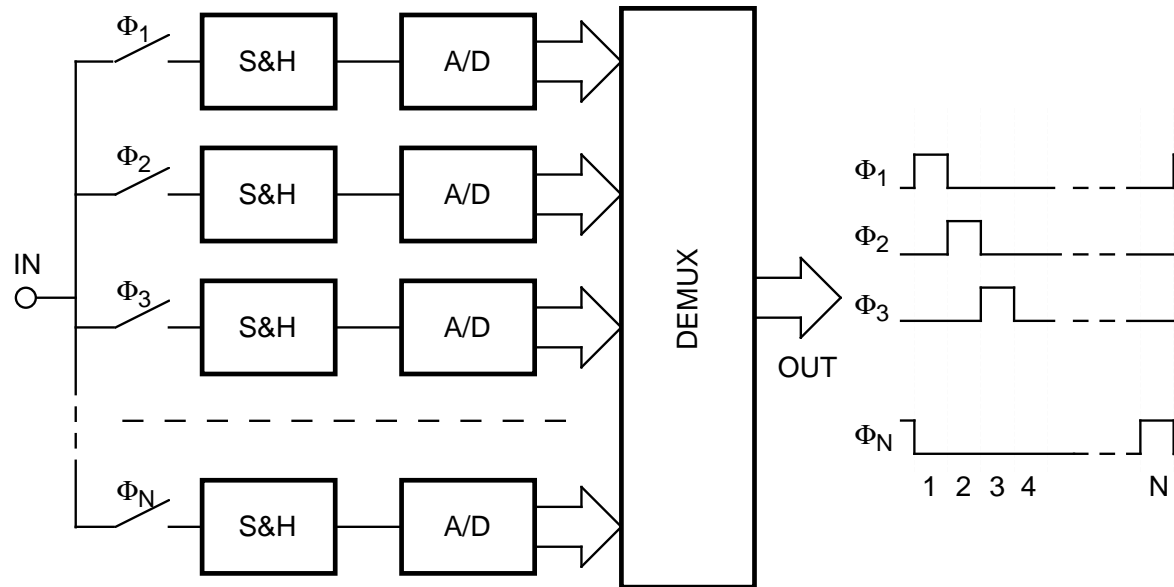- ❑ The conversion speed increases by using N A/D converters **interleaved**
- ❑ The **analog multiplexer** placed at the input of the circuit connects sequentially the input terminal to one of the **conversion channels**



INTERLEAVED A/D CONVERTERS

- ❑ The **sampling rate** of the input is $1 / T$ while the time allowed for the **conversion** in each channel (including the sampling) is $N T$
- ❑ The converters work with at N times **lower sampling rate** than the system
- ❑ The **digital multiplexer** at the output receives the digital results from the **slow converters** and provides the interleaved output at the full **data rate**
- ❑ The interleaved architecture allows **slow converters** to be used but requires **full speed** operation in the **Sample and Hold (S&H)**
- ❑ The input signal must be sampled with an **error** smaller than $1 / 2$ **LSB** during the sampling period T




INTERLEAVED A/D CONVERTERS

- ❑ **Limitations** of interleaved A/D converters
 - ☹ If one conversion channel is affected by an **error**, every N clock cycles the output changes → **Spur signal** at frequency f_S / N
 - ☹ Often, the **sampling frequency** ($f_S = 1 / T$) is slightly higher than the **Nyquist limit** → The spur signal falls in the signal band causing a degradation of the SNR
 - ☹ The non-idealities that are often responsible of the above described distortion are gain error and offset
- ❑ **Solution** → Use analog or digital **calibration** on-line or off-line, eventually **self-calibration**, to correct the errors



PIPELINE A/D CONVERTERS

 - ❑ **Pipeline** A/D converter → **Cascade** of stages operating in **parallel** each producing one or more bits
- ❑ Bits relative to **successive input samples** are determined during the same clock cycle
- ❑ The **sampling rate** increases at the expense of a system **latency**




PIPELINE A/D CONVERTERS

- ❑ The **signal processing** in the analog path must preserve the information content of the **residual bits**
- ❑ The circuit **complexity** and the **power consumption** in a pipeline stage are significantly lower than in a complete data converter
- ❑ The pipeline architecture achieves a better **trade-off** between **speed**, **area** and **power consumption** with respect to the interleaved architecture
- ❑ The total number of **stages** K required to obtain a given resolution decreases as the **number of bits** of each stage increases, but the **analog processing** required for each stage also increases at the expense of speed and the power consumption → **Trade-off**




PIPELINE A/D CONVERTERS

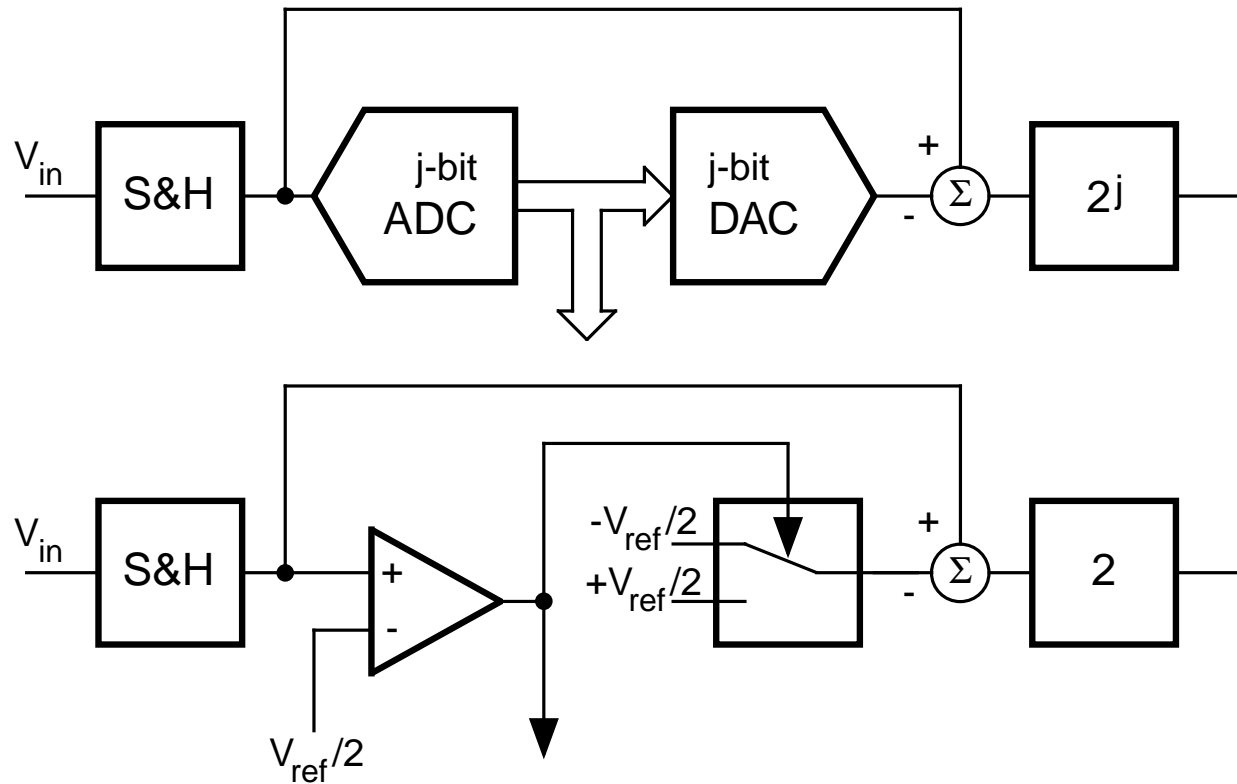- Typically **few bits per stage** are used → **CMOS** switched capacitor implementation of a **one bit per stage** pipeline A/D converter



PIPELINE A/D CONVERTERS

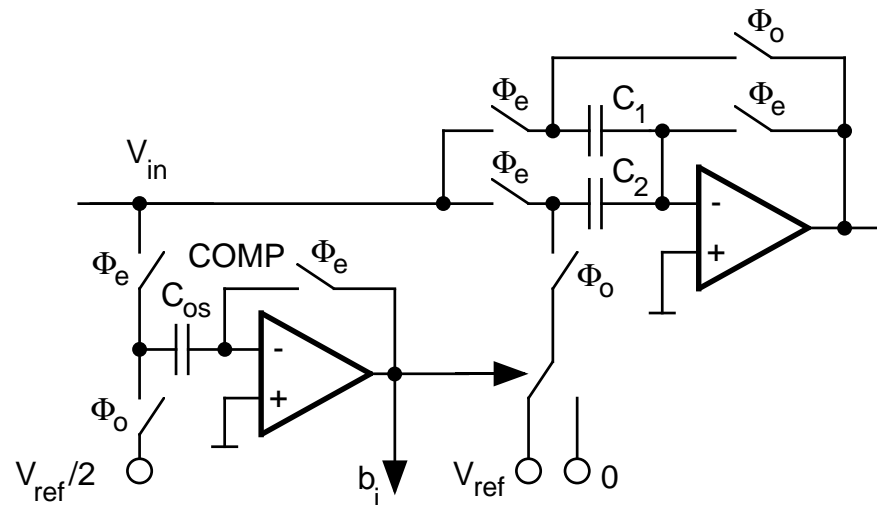- During the **even clock phase** Φ_e the circuit **samples** the input voltage on two equal capacitors C_1 and C_2 and the **comparator** performs the **auto-zero** by storing the offset on capacitor C_{os}
- During the **odd clock phase** Φ_o capacitor C_1 is connected in **feedback** \rightarrow C_1 receives the charge delivered by C_2



PIPELINE A/D CONVERTERS

- ❑ The **charge transfer** between C_1 and C_2 is **offset insensitive** since they have been pre-charged to the offset of the amplifier
- ❑ The left plate of the auto-zero capacitor switches toward the **threshold voltage** $V_{\text{ref}} / 2$ → The amplifier, operated in **open-loop** condition, provides the **bit value**
- ❑ The 1-bit DAC charges C_2 with V_{ref} or 0 , depending on the **bit value** → The analog output is given by

$$V_{\text{out}} = V_{\text{in}} \left(1 + \frac{C_2}{C_1} \right) - b_j V_{\text{ref}} \frac{C_2}{C_1}$$

- ❑ Capacitors C_1 and C_2 are **equal** → The circuit **multiplies** the input by **two**




OVERSAMPLED A/D CONVERTERS

- ❑ The **effective number of bits** of an A/D converter can be increased by using **oversampling** techniques
- ❑ If the **sampling frequency** is higher than the **Nyquist limit** only a **fraction** of the quantization noise power falls in the **signal band**
- ❑ A **digital filter** which rejects the **out-of-band noise** is required to increase the effective number of bits
- ❑ **Modern technologies** allow higher and higher frequency of **operation** either in **digital** and in **analog** sections → For signals with a relatively small band it is possible to trade **speed** with **resolution**
- ❑ **Oversampling ratio** → OSR




SIGMA-DELTA MODULATORS

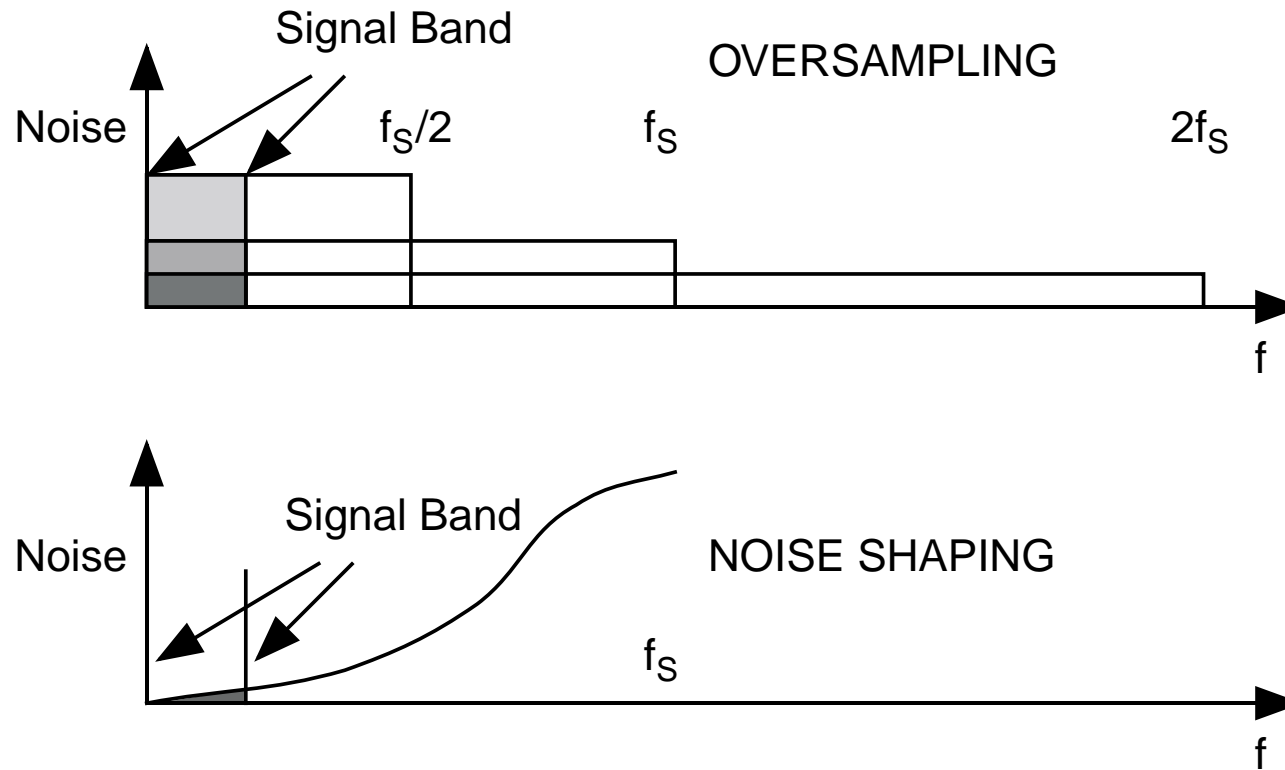- ❑ **Noise shaping** → Reduce the amount of **quantization noise** in the signal band, thus increasing the **signal-to-noise ratio**



NOISE SHAPING

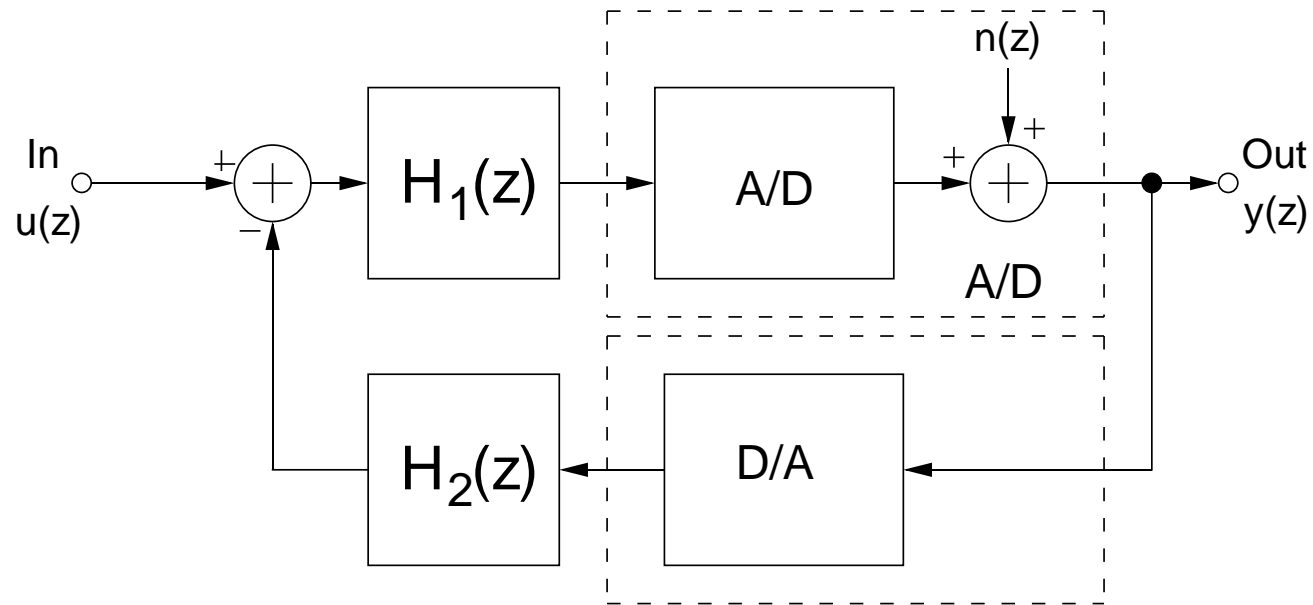- ❑ **Quantizer** included in the **feedback loop**
 - Two **inputs** (signal and quantization noise) and one **output**
 - Different transfer functions for the **signal** and the **quantization noise**



SIGNAL AND NOISE TRANSFER FUNCTIONS

$$\square y(z) = \frac{H_1(z)}{1 + H_1(z)H_2(z)}u(z) + \frac{1}{1 + H_1(z)H_2(z)}n(z)$$

$$\square \text{Signal transfer function} \rightarrow \text{STF}(z) = \frac{H_1(z)}{1 + H_1(z)H_2(z)}$$

$$\square \text{Noise transfer function} \rightarrow \text{NTF}(z) = \frac{1}{1 + H_1(z)H_2(z)}$$

\square **Typical** architecture

$$\rightarrow \text{STF}(z) = 1$$

$$\rightarrow \text{NTF}(z) = (1 - z^{-1})^L, L \rightarrow \text{Order of the sigma-delta modulator}$$






FIRST ORDER SIGMA-DELTA MODULATOR

❑ **Single bit** A/D and D/A converters

❑ $H_1(z) \rightarrow$ Integrator

$$H_1(z) = z^{-1} / (1 - z^{-1})$$

❑ $H_2(z) \rightarrow 1$

  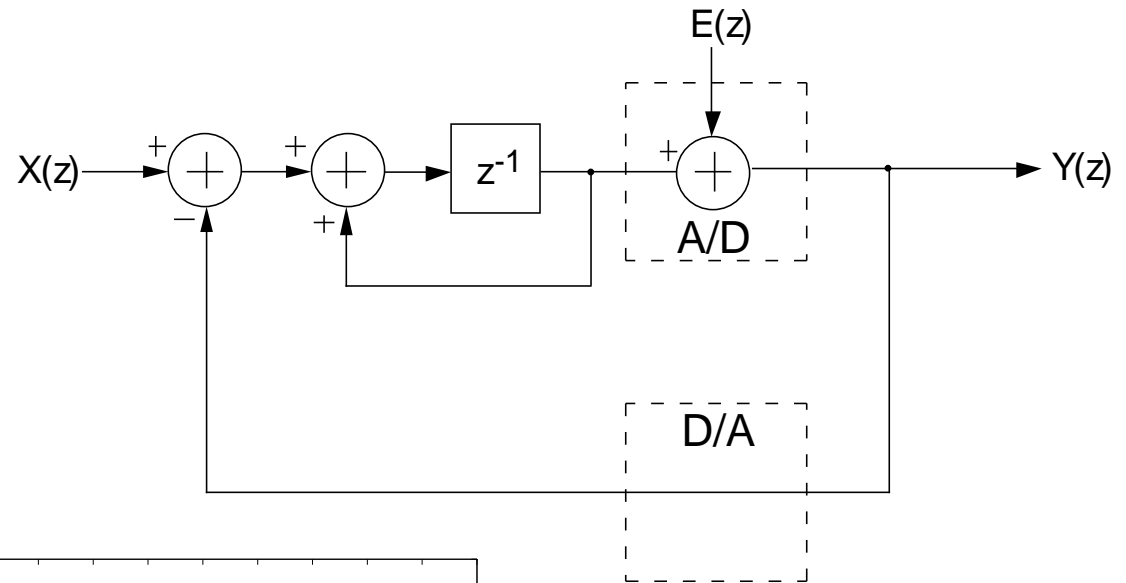

$$NTF(z) = (1 - z^{-1})$$



FIRST ORDER SIGMA-DELTA MODULATOR

$$\square \text{NTF}(z) = (1 - z^{-1}) = (1 - e^{-j\omega T_s}) = e^{-j\omega T_s/2} 2j \sin(\omega T_s/2)$$

$$\square P_{\text{noise}} = \int_0^{f_B} \frac{P_Q(f)}{1/(2T_s)} \text{NTF}(f)^2 df \approx P_Q \frac{\pi^2}{3} (2f_B T_s)^3 = P_Q \frac{\pi^2}{3} \text{OSR}^{-3}$$


\square For an **input sinewave** the RMS signal power is $\Delta^2/8$ and the **SNR** becomes

$$\text{SNR} = 10 \log \frac{\text{OSR}^3 \Delta^2}{8 \left(\frac{\Delta^2}{12}\right) \left(\frac{\pi^2}{3}\right)} = -3.14 + 9.03 \log_2(\text{OSR}) = 6.02N$$




SECOND ORDER SIGMA-DELTA MODULATOR

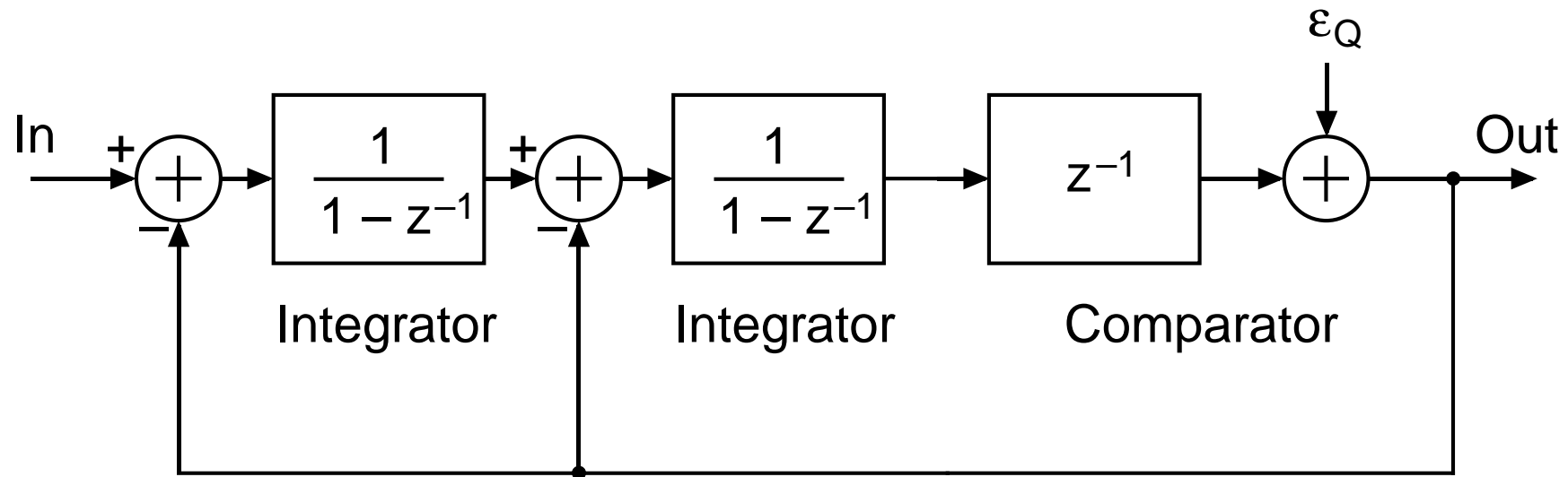- ❑ **Two integrators** around the feedback loop
- ❑ **Signal** transfer function \rightarrow $STF(z) = z^{-1}$
- ❑ **Noise** transfer function \rightarrow $NTF(z) = (1 - z^{-1})^2$




SECOND ORDER SIGMA-DELTA MODULATOR

 - ❑ **Two integrators** around the feedback loop
- ❑ **Signal** transfer function \rightarrow $STF(z) = z^{-2}$
- ❑ **Noise** transfer function \rightarrow $NTF(z) = (1 - z^{-1})^2$




SECOND ORDER SIGMA-DELTA MODULATOR

Switched-capacitor implementation

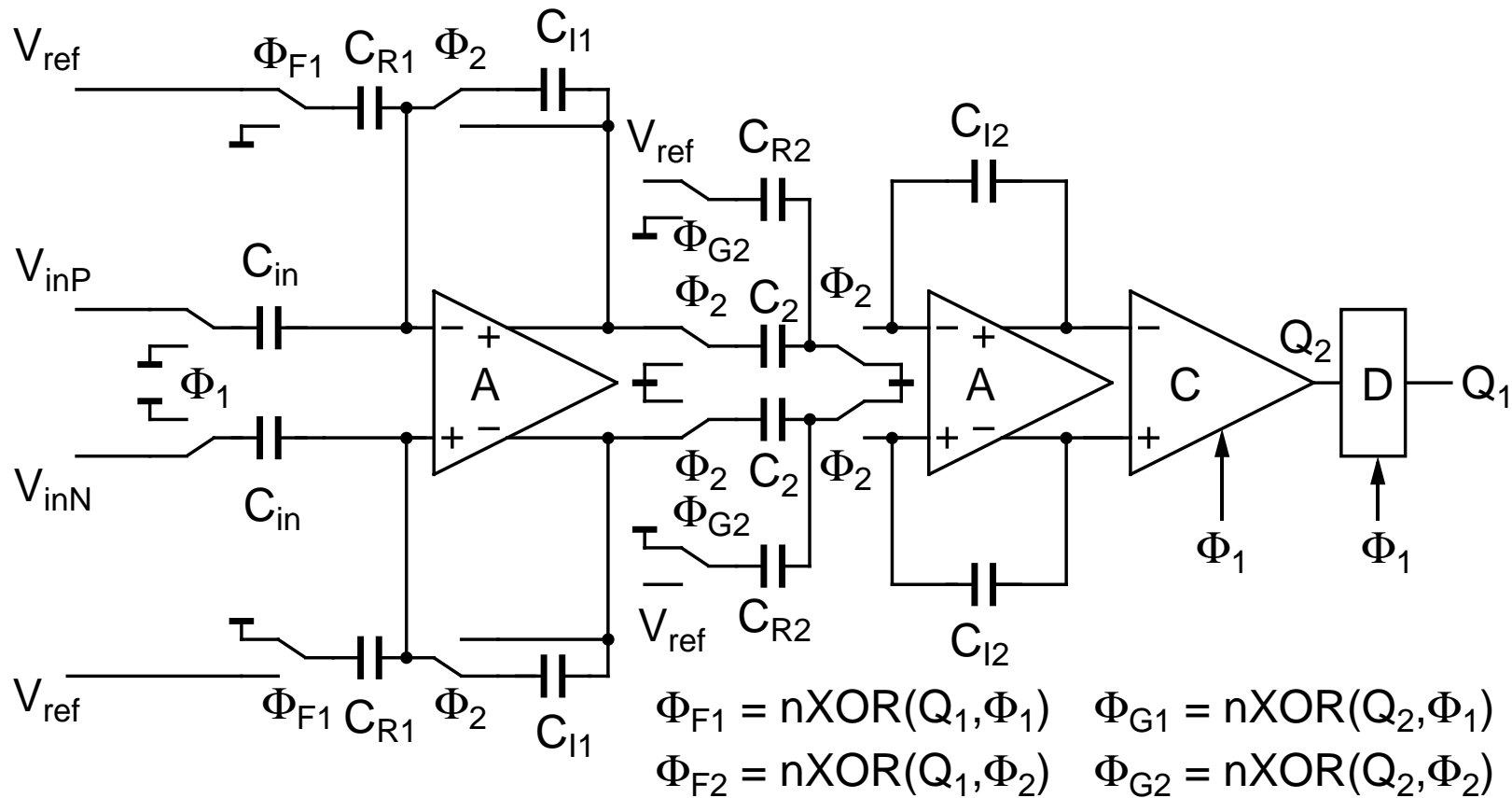


NOISE SHAPING

 - The **in-band** noise is reduced, while the **out-of-band** noise is enhanced




INTEGRATOR OUTPUT SWING

Second Order Sigma-Delta Modulator

 

First Integrator

 


Second Integrator



SIGNAL-TO-NOISE RATIO VS INPUT AMPLITUDE

Second Order Sigma-Delta Modulator

 

QUANTIZATION NOISE POWER

- **In-band** noise power for an **Lth-order** sigma-delta modulator

$$P_Q = \frac{\Delta^2 \pi^{2L}}{2^{2N} (2L + 1) 3 \text{OSR}^{(2L + 1)}}$$
$$\text{SNR} = \frac{2^{2N} (2L + 1) 3 \text{OSR}^{(2L + 1)}}{2 \pi^{2L}}$$

↳ Δ → Full scale voltage, N → Number of bits of the quantizer,
 L → Order of modulator, OSR → Oversampling ratio,
Signal amplitude → $\Delta^2/8$

- The **in-band quantization noise** decreases **$3(2L + 1)$ dB** per octave of oversampling and 6 dB per additional bit of quantizer resolution



SIGMA-DELTA MODULATOR NON-IDEALITIES

- Clock Jitter
- Integrator thermal and $k T / C$ noise
- Operational amplifier finite gain
- Operational amplifier finite bandwidth
- Operational amplifier finite slew-rate
- Continuous-time vs switched-capacitor and single-bit vs multi-bit



CLOCK JITTER


- ❑ **SC $\Sigma\Delta$ modulator** → Sampled data system
 - ↳ The **clock jitter** effect is restricted to the **input signal sampling**
 - ↳ Sampling clock jitter → **Non-uniform sampling**
 - ↳ The **error** introduced is a function of both the **input signal** and the **statistical properties** of the jitter
- ❑ **Error** due to a **clock jitter δ** when sampling a sinusoidal signal **$x(t)$** with amplitude **A** and frequency **f_{in}**
 - ↳ $x(t + \delta) - x(t) \approx 2\pi f_{in} \delta A \cos(2\pi f_{in} t) = \delta \frac{d}{dt}x(t)$
 - ↳ **Gaussian** clock jitter with **standard deviation $\Delta\tau$** → **White noise** with power $P_j = (2\pi f_{in} \Delta\tau A)^2 / 2$, integrated from 0 to $f_s / 2$



SWITCHED-CAPACITOR INTEGRATOR NOISE

- ❑ **Noise sources** in a SC $\Sigma\Delta$ modulator
 - ➔ Thermal noise in the sampling switches of the integrators
 - ➔ Intrinsic noise of the operational amplifiers
 - 😊 Large **DC gain** of the first integrator ➔ Noise performance determined by the **input stage**

SC Integrator

 


$$\text{Integrator Gain} \rightarrow \beta = \frac{C_S}{C_F}$$

$$e_T^2 = \int_0^{\infty} \frac{4kTR_{on}}{1 + (2\pi fR_{on}C_S)^2} df = \frac{kT}{C_S}$$




SWITCHED-CAPACITOR INTEGRATOR NOISE

 


- Main noise source $\rightarrow k T / C$
- SC integrator \rightarrow Time variant network



$$N = \int_0^\infty |NTF|^2 S_N df$$

 

Integration Phase (2)

 

SWITCHED-CAPACITOR INTEGRATOR NOISE

- ❑ **Sampling** phase (1)
- ❑ **Noise Sources** $\rightarrow S_{N,S} = S_{N,R} = 4kTR_{on}$
- ❑ $NTF_{S,1} = \frac{1}{1 + sC_S R_{on}}$
- ❑ $NTF_{R,1} = \frac{1}{1 + sC_R R_{on}}$
- ❑ **Total Power** $\rightarrow N_1 = \frac{2kT}{C}$ with $C_S = C_R = C$



SWITCHED-CAPACITOR INTEGRATOR NOISE

□ **Integration** phase (2)

□ **Noise Sources** $\rightarrow S_{N,O} = \frac{4kT(1 + \gamma)}{3g_m}$, $S_{N,S} = S_{N,R} = 4kTR_{on}$

□ $NTF_{S|R,2} = -\frac{1}{2} \frac{\eta g_m + sC_L}{\eta g_m + s(2C_L + 2C + \eta g_m R_{on}) + s^2 C C_L R_{on}}$

□ $NTF_{O,2} = \frac{\eta g_m}{\eta g_m + s(2C_L + 2C + \eta g_m R_{on}) + s^2 C C_L R_{on}}$

□ **Total Power** $\rightarrow N_2 = \frac{2kT(2C + C_L + 2\gamma C + \eta g_m R_{on} C)}{C(2C + 2C_L + \eta g_m R_{on} C)}$




SWITCHED-CAPACITOR INTEGRATOR NOISE

- Combining all of the **noise contribution** from both clock phases, we obtain the **total thermal noise power**
- **Total Power** $\rightarrow N_{Th} = \frac{2kT(4C + 3C_L + 2\gamma C + 2\eta g_m R_{on} C)}{C(2C + 2C_L + \eta g_m R_{on} C)}$
- **In-Band Power** $\rightarrow P_{Th} = \frac{2kT(4C + 3C_L + 2\gamma C + 2\eta g_m R_{on} C)}{OSRC(2C + 2C_L + \eta g_m R_{on} C)}$
- Typical values of the **parameters** $\rightarrow \gamma = 4, \eta = 3, g_m = 750 \text{ mS}$ and $R_{on} = 1 \text{ k}\Omega$



CONTINUOUS-TIME INTEGRATOR NOISE

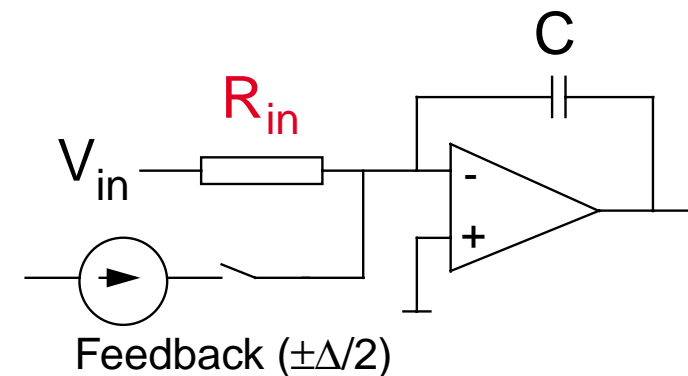- The **thermal noise** generator of the **input resistance** is in series with the input signal → The **noise power** in the signal band B is
$$v_n^2 = 4kTR_{in}B$$
- Upper **limit of R_{in}** → $R_{in} < \Delta^2 / (4kTB10^{SNR/10})$
- Lower **limit of C** → $C > T_s(4kTB10^{SNR/10}) / \Delta^2$
- The **operational amplifier** noise is treated as usual in continuous-time circuits



OPERATIONAL AMPLIFIER FINITE GAIN

- ❑ If the **operational amplifier** has **finite gain** A_0 the voltage of the non-inverting input is not analog ground but $-V_o / A_0$
- ❑ The **transfer function** of a SC integrator becomes


$$H(z) = \frac{C_S / C_F}{\left(1 + \frac{1}{A_0} + \frac{C_S / C_F}{A_0}\right)z - \left(1 + \frac{1}{A_0}\right)}$$

- ☹ The integrator shows a **gain error** (not particularly important) and a **phase error**
- 😊 The problem can be alleviated with specific **circuit solutions** (similar to auto-zero)



OPERATIONAL AMPLIFIER SETTLING

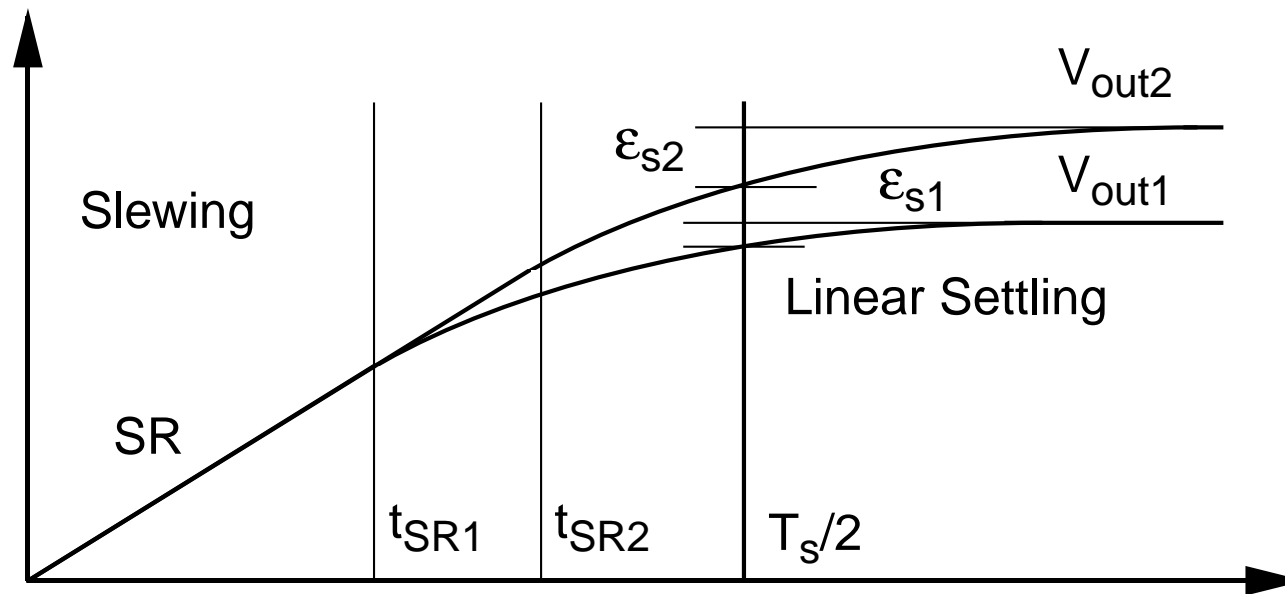- ❑ When the differential input voltage of the **operational amplifier** exceeds the **overdrive** voltage of the input stage → **Slewing**
- ❑ The **slew-rate** SR and the **bandwidth** $GBW = 1 / (2 \pi \tau)$ of the **operational amplifier** determine the **settling error**



OPERATIONAL AMPLIFIER SETTLING

□ Operational amplifier settling model

$$\rightarrow V_{\text{out}}(t) \approx V_{\text{out}}(0) + \text{SR}t_{\text{SR}} + \alpha V_{\text{OV}} \left(1 - e^{-\frac{(t-t'_{\text{SR}})}{\tau}} \right) \quad \text{for } t > t_{\text{SR}}$$

→ **Single pole** model

→ Time $t = 0$ corresponds to the **beginning** of each **clock period**

→ Parameters α and t'_{SR} model a **smooth transition** at $t = t_{\text{SR}}$

→ The **slewing time** depends on the **input signal**

→ The **settling region** depends on $T_S / 2 - t_{\text{SR}}$

$$\varepsilon_S(n) = V_{\text{OV}} e^{-\frac{T_S}{2\tau} + \frac{\alpha(V_{\text{in}}(n) - V_{\text{OV}})}{\text{SR}\tau}} \quad \text{where } \alpha = C_S / C_F$$



OPERATIONAL AMPLIFIER SETTLING

□ Spectrum of the settling error

$$P_{\varepsilon_s} df = \frac{(\varepsilon_{\max})^2}{12f_s} df \quad f \leq \frac{f_s}{2}$$

- ↳ The error ε_s is not correlated with the input signal
- ↳ The error ε_s is uniformly distributed from 0 to ε_{\max}
- ↳ The probability distribution function of ε_s is uniform

□ The settling error power in the signal band is

$$v_s^2 = \frac{V_{ov}^2}{3OSR} e^{-2\left[\frac{1}{2BOSR\tau} - \frac{\alpha\Delta}{SR\tau}\right]}$$



OPERATIONAL AMPLIFIER SETTLING

- ❑ The **time** allowed for the **slewing phase** must be a small part (k) of the clock period $\rightarrow T_S / 2 > k \Delta / SR$ (slew-rate design guideline)
- ❑ For a given **signal bandwidth** B and **operational amplifier bandwidth** $GBW = 1 / (2 \pi \tau)$, the settling error becomes dominant above a given **oversampling**
- ❑ Design **guidelines**

$$\rightarrow V_{ov}^2 = \frac{I_D}{K' \frac{W}{L}} \text{ and } \tau = \frac{C_0}{g_m} = \frac{C_0 V_{ov}}{2I_D}$$

- ☹ The **drain current** in the input pair must be very large



CONTINUOUS TIME VS SWITCHED CAPACITOR

- ❑ **Continuous time** sigma-delta modulators
 - 😊 The **current** at the input of the first integrator is **continuous-time** → The **slew-rate** requirement is less critical
 - 😊 The input resistance can be external → Very linear and trimmed to the proper value
 - 😞 The **clock jitter** in the **feedback** DAC is critical
 - 😞 The **time constant** of the integrator ($R C$) varies with the process → The modulator **transfer function** changes
 - 😞 The **feedback DAC** requires a very accurate **current** or **charge** source, which may increase significantly the **power consumption**




SINGLE-BIT VS MULTI-BIT

- ❑ **Multi-bit** sigma-delta modulators
 - 😊 The **quantization noise** is lower
 - 😊 The **quantization noise** model is more accurate
 - 😊 The **error signal** is smaller → Reduced integrator **output swing**, better **stability**
 - 😊 **Lower modulator order** for the same resolution → Simpler **decimator**
 - 😞 The modulator is more **complex**
 - 😞 The **power consumption** increases
 - 😞 The DAC is not inherently **linear**
 - 😞 **Multi-bit** output flow



INCREMENTAL ADC

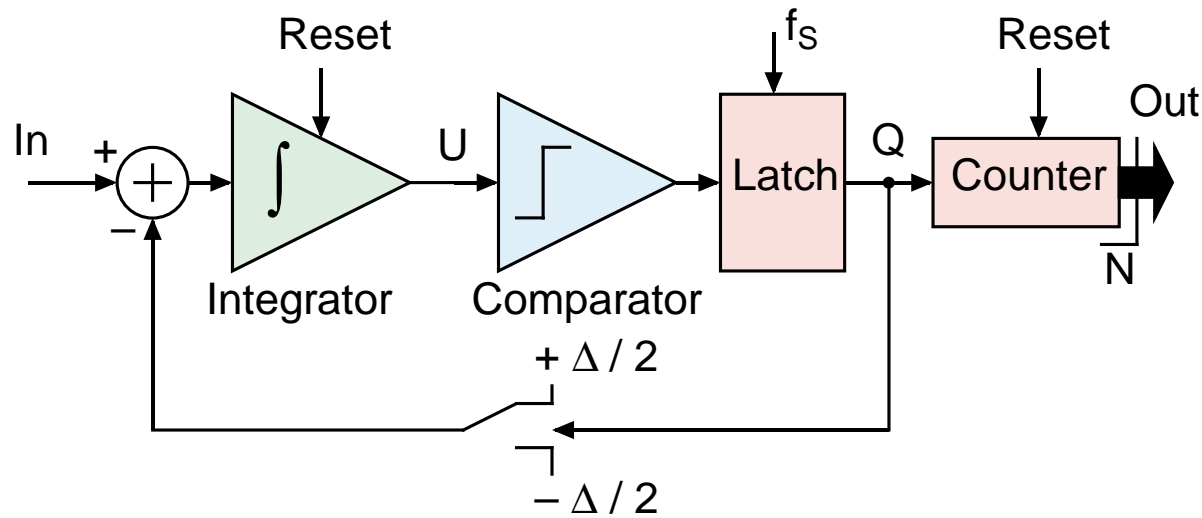

Digital Output

- $Out = 2^{N+1} \frac{In}{\Delta}$
- ➔ $N \rightarrow$ Resolution
- ➔ $\Delta \rightarrow$ Full scale


□ Conversion algorithm

$$\begin{cases} U(k+1) = U(k) + [In - (-1)^{Q(k)+1} \Delta/2] , 0 \leq k \leq 2^N \\ U(0) = In \end{cases}$$



D/A CONVERSION FUNDAMENTALS

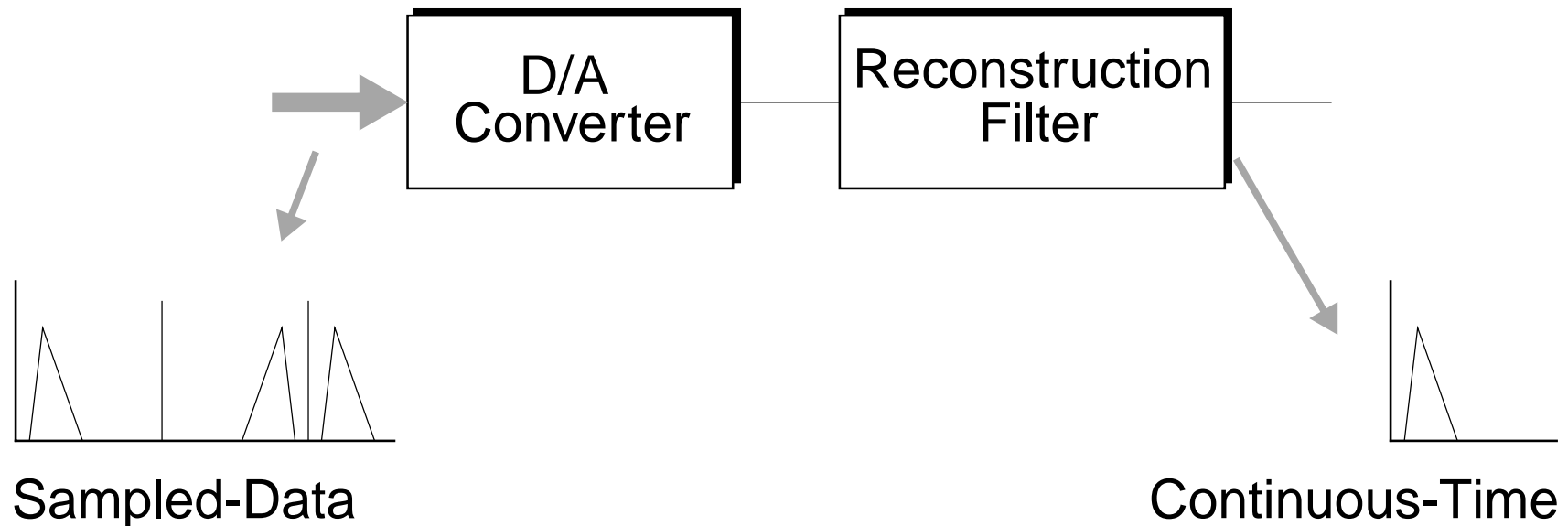- A **D/A converter** transforms a **digital sampled-data** signal into an **analog continuous-time** signal
 - ↳ Domain transformation
 - ↳ Reconstruction



D/A CONVERSION FUNDAMENTALS

- The conversion from **digital to analog** does not change the **spectrum** of the signal

- A **cardinal hold** performs the **ideal reconstruction**

$$R(\omega) = 1 \quad \text{for} \quad \omega \leq \omega_S/2; \quad 0 \quad \text{otherwise}$$

$$r(t) = \frac{\sin(\omega_S t/2)}{\omega_S t/2}$$

- ☹ The cardinal hold can not be practically realized

- A zero-order **hold** performs the **approximate reconstruction**


$$h(t) = 1 \quad \text{for} \quad 0 < t < T; \quad 0 \quad \text{otherwise}$$

$$H(\omega) = (1 - e^{j\omega T}) / (j\omega)$$



D/A CONVERSION FUNDAMENTALS

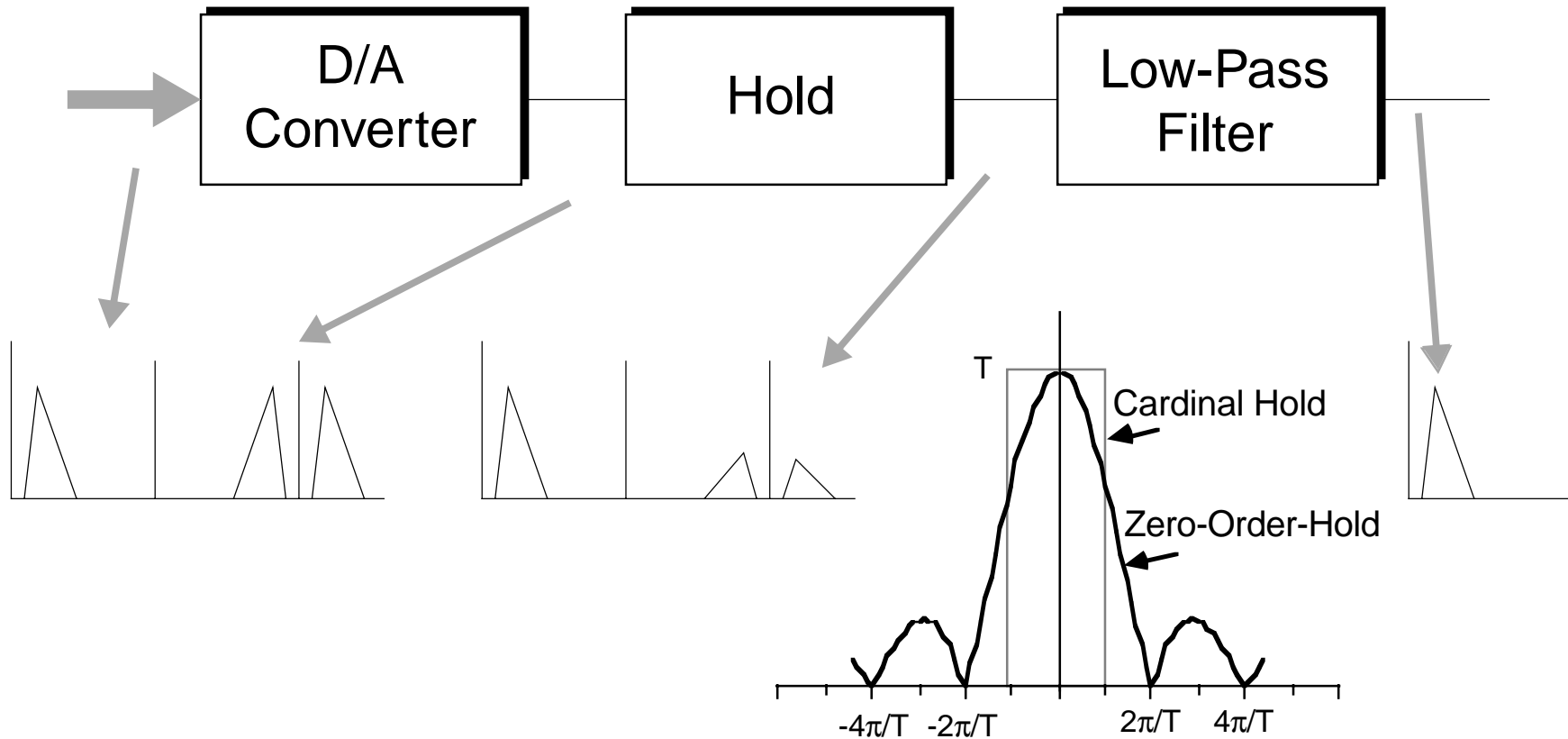- **Approximate reconstruction** with zero-order hold



D/A CONVERTER BUILDING BLOCKS

- ❑ The implementation of any **conversion algorithm** requires **active elements** and **passive components**
 - ↳ **Measurement** or **attenuation** of analog variables
- ❑ **Accuracy** and **stability** of attenuation and measurement elements strongly affect the overall performance of the **D/A converter**
 - ☹ **Mismatches** are responsible for most of the **linearity** errors (differential and integral)
- ❑ The **matching** accuracy of **integrated resistors** is of the order of 0.1%-0.4% → **Resolution** up to 9-10 bits
 - ↳ Careful **layout** of the circuit
 - ↳ **Interdigitated** structures with **dummies** at the edges



D/A CONVERTER BUILDING BLOCKS

- ❑ The **matching** accuracy of **integrated capacitors** is of the order of 0.05%-0.2% → **Resolution** up to 10-12 bits
 - ↳ Careful **layout** of the circuit
 - ↳ **Common centroid** structures with **dummies** at the edges
- ❑ **Capacitor** based D/A converters require analog **switches**
 - ↳ In **CMOS** technology **switches** are easily implemented with a single transistor or a pair of complementary transistors
 - ↳ The **on-resistance** is inversely proportional to the transistor **aspect ratio** and on the **overdrive voltage** applied ($V_{GS} - V_{th}$)
 - ☹ Limitation → **Clock feedthrough**
- ❑ **Active elements** → Operational amplifiers




D/A CONVERTER ARCHITECTURES

- Resistive and capacitive D/A converters
- Charge redistribution D/A converters
- Multiplying D/A converters
- Algorithmic D/A converters
- Current steering D/A converters
- Sigma-delta D/A converters



RESISTIVE LADDER D/A CONVERTERS

 - The input **digital word** controls the analog **switches**




- **Limitations** → Resistor **mismatches** and **distortion** from non-linear amplification of offset and low-frequency noise




MOS CURRENT DIVIDER D/A CONVERTERS

 - Two equal MOS transistors in parallel divide in equal parts the reference current independently of the non-linear response




CAPACITIVE DIVIDER D/A CONVERTERS

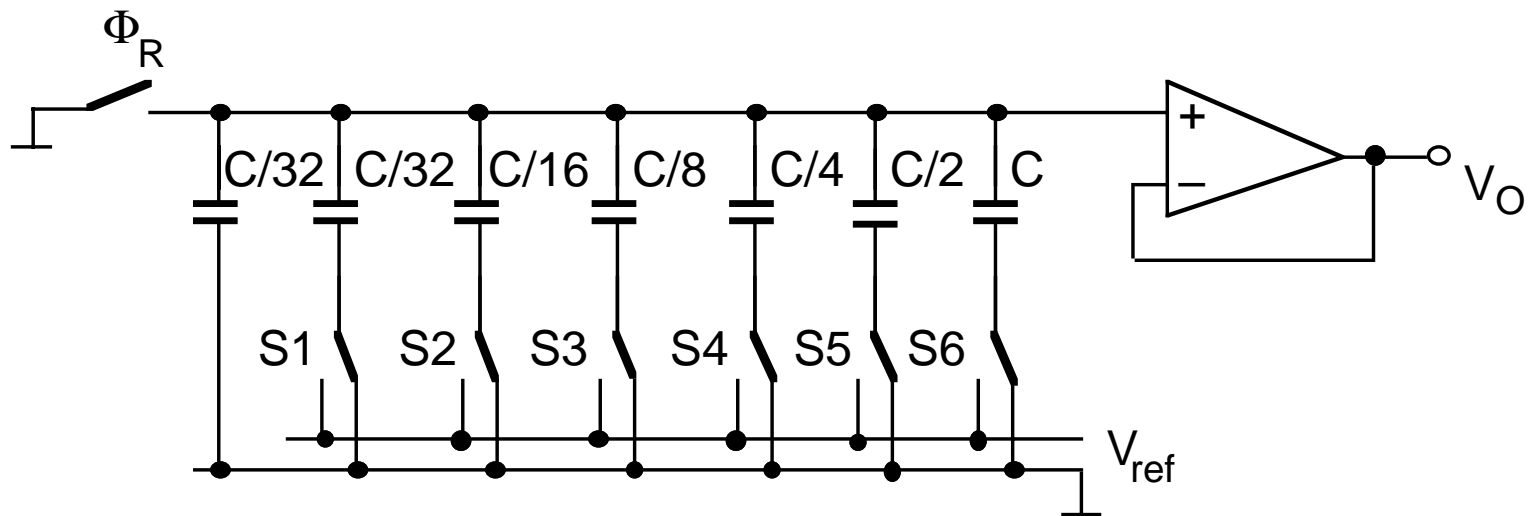- ❑ The capacitors are **reset** (Φ_R) before each **conversion**
- ❑ The input **digital word** controls the analog **switches**
- ❑ The capacitors are **binary weighted**
 - ☹ For **high resolution** the unity capacitance is very small




CAPACITIVE DIVIDER D/A CONVERTERS

 - ❑ High resolution → Use of an attenuating capacitor
- ❑ The unity capacitance is multiplied by a factor $k = 32$
- ❑ Attenuating capacitor → $C_{ATT} = C_1 / (k - 1)$




RESISTIVE DIVIDER D/A CONVERTERS

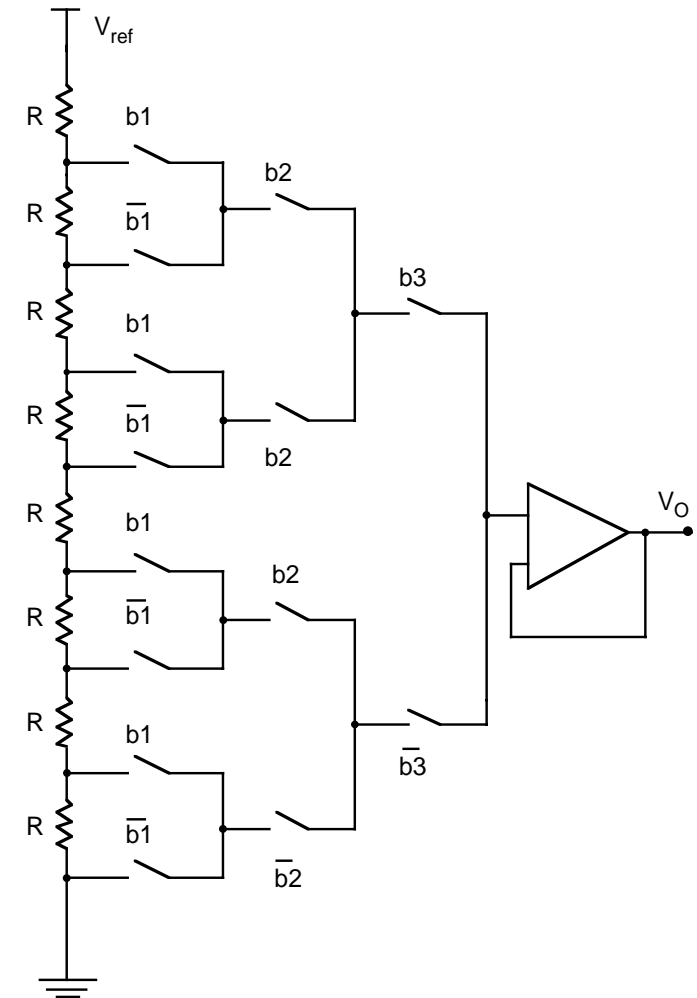- ❑ The **reference voltage** is divided by a string of equal **resistors**
- ❑ A particular **voltage tap** is selected with a **tree** of switches
- ❑ The **input impedance** of the buffer is very high
- ❑ Features
 - 😊 Intrinsically **monotonic**
 - 😞 Sensitive to the buffer **offset**
 - 😞 **Delay** due to several switches in series




RESISTIVE DIVIDER D/A CONVERTERS

 - ❑ **Folded** resistive string
- ❑ **Parallel selection** of 8 different voltage taps
- ❑ **Tree** of switches to select one of the 8 voltage taps
- ❑ Features
 - 😊 Intrinsicly **monotonic**
 - 😞 **Corner** resistors difficult to implement
 - 😊 **Compact** layout




RESISTIVE DIVIDER D/A CONVERTERS

 - ❑ Resistor matrix divides the reference voltage (XY selection)
- ❑ Output buffer required
- ❑ Features
 - 😊 High speed
 - 😊 Intrinsically monotonic
 - 😊 Up to 10 bits of resolution
 - ☹ Limitations due to the output buffer




CHARGE REDISTRIBUTION D/A CONVERTERS

 - ❑ The **charge** stored the capacitive array during one clock **phase** is **redistributed** in the entire array during the other clock **phase**
 - 😊 **Offset** insensitive architecture
 - 😞 **Output** available only during one clock **phase**




RESISTIVE AND CAPACITIVE D/A CONVERTERS

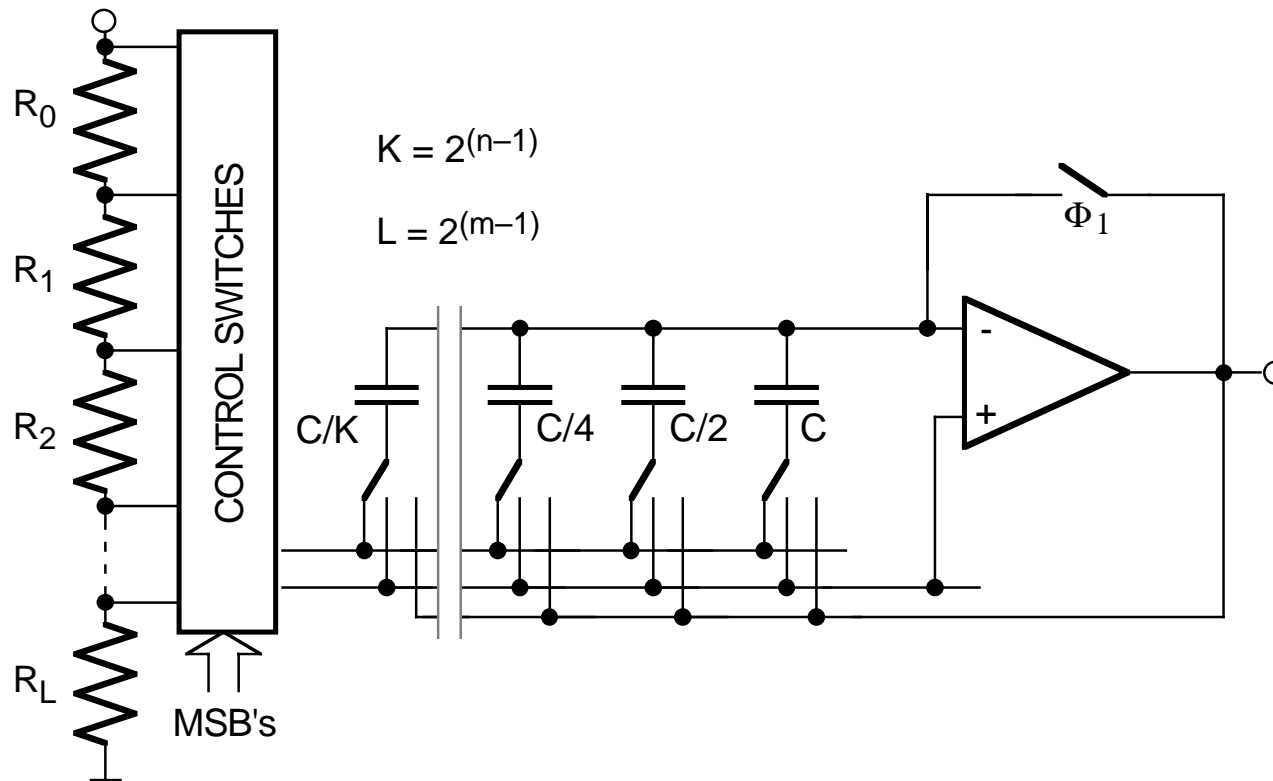- The m **MSBs** are provided by a **resistive divider** DAC while the n **LSBs** are provided by a capacitive **charge redistribution** DAC




MULTIPLYING D/A CONVERTER

 - ❑ The **charge** stored in the **array** in one clock **phase** is **injected** into the **feedback** capacitor during the other clock **phase**
- ❑ Features
 - 😊 Inverting or non-inverting
 - 😊 **Offset** insensitive




ALGORITHMIC D/A CONVERTERS

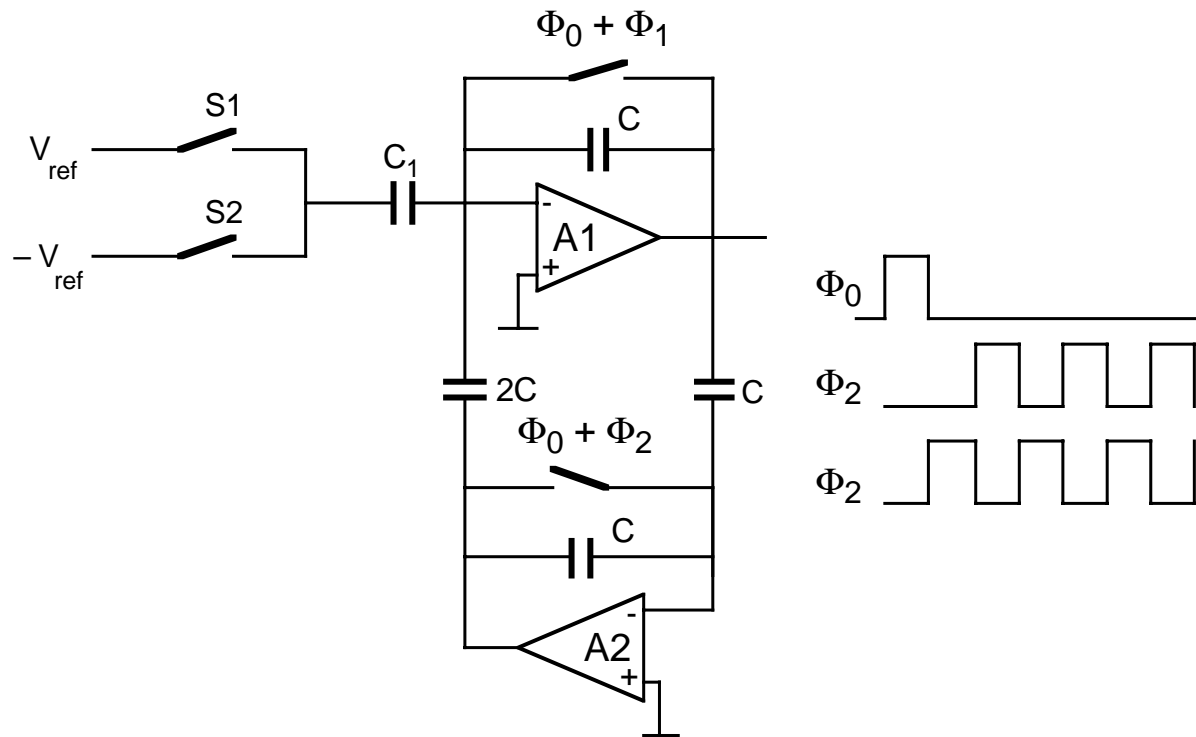- ❑ The **analog output** is built in **N successive** clock cycles
- ❑ During each **clock cycle** the voltage in the loop is **multiplied** by 2




ALGORITHMIC D/A CONVERTERS

 - ❑ **Exact** multiplication by 2
 - ➔ **Integrate** the input signal **two times**




- ➔ **Exchange** capacitors C_1 and C_2

 

CURRENT STEERING D/A CONVERTERS

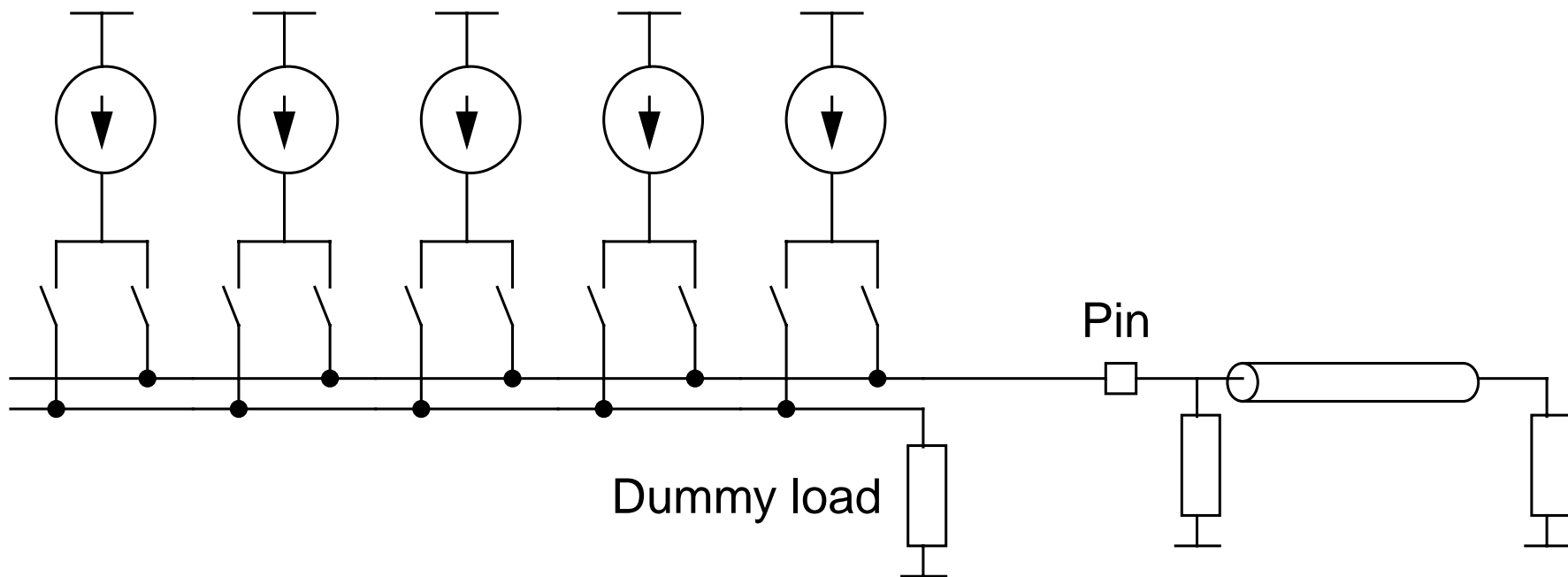- ❑ Suitable for very **high speed** applications (several tens of MHz)
- ❑ A **current** proportional to the input **digital word** is injected into the external **resistive load** (termination resistance)




CURRENT STEERING D/A CONVERTERS

- Current steering D/A converters **design issues**
 - ↳ **Binary weighted** current sources or **equal** current sources
 - ↳ **Switch** on and off the current sources → Switching **glitches**
 - ↳ **Matching** between current sources
- Current steering D/A converters **implementation issues**
 - ↳ **Output** resistance
 - $$I_D = \mu C_{ox} (W/L) (V_{GS} - V_{Th})^2 (1 + \lambda V_{DS})$$
$$I_C = I_0 e^{(qV_{BE})/(kT)} (1 + V_{CE}/V_A)$$
 - ↳ **Voltage drop** on the power supply line → **Mirror** current sources **locally** and distribute currents



SIGMA DELTA D/A CONVERTER

 - ❑ Audio applications (CD players)
- ❑ The N -bit input digital word is truncated to M -bits ($M < N$) and the sampling frequency is increased
 - ➔ Digital interpolation filter and digital sigma-delta modulator
 - 😊 Oversampling and noise-shaping
 - ➔ M -bit D/A converter and reconstruction low-pass filter
- ❑ Trade-off between accuracy, speed and complexity



REFERENCES

A/D Conversion Fundamentals

- F. Maloberti, J. Franca, R. S. Soin, "Analogue-Digital ASICs", Peter Peregrinus, London, UK, 1991.
- David A. Johns, Ken Martin, "Analog Integrated Circuit Design", John Wiley, New York, USA, 1997.
- Rudy van de Plassche, "Integrated Analog-To-Digital and Digital-To-Analog Converters", Kluwer Academic Publishers, Dordrecht, The Netherlands, 1994.
- A. B. Grebene, "Bipolar and MOS Analog Integrated Circuits Design", John Wiley, New York, USA, 1984.
- Analog Devices, "Analog-Digital Conversion Handbook", Prentice Hall, New Jersey, USA, 1986.
- R. L. Geiger, P. E. Allen, N. R. Strader, "VLSI design Techniques for Analog and Digital Circuits", Mc Graw Hill, New York, USA, 1990.
- F. Maloberti, F. Francesconi, P. Malcovati and O. J. A. P. Nys, "Design Considerations on Low-Voltage Low-Power Data Converters", IEEE Transactions on Circuits and Systems, vol. 42, pp. 853-863, Nov. 1995.



REFERENCES

- V. Liberali, S. Brigati, F. Francesconi, F. Maloberti, “Progress in High-Speed and High-Resolution CMOS Data Converters”, *Microelectronics and Reliability*, vol. 37, pp. 1411-1420, Sept. 1997

Full Flash and Two-Step Flash A/D Converters

- K. Ono, “BiCMOS Flash A/D Converter, FCDL Error Suppressing Encode Logic”, *IEEE Journal of Solid-State Circuits*, vol. 30, pp. 1460-1464, Sept. 1997.
- M. Yotsuyanagi, H. Hasegawa, M. Yamaguchi, M. Ishida, K. Sone, “A 2 V 10 bit 20Ms/s Mixed-Mode Subranging CMOS A/D converter”, *IEEE Journal of Solid-State Circuits*, vol. 30, pp. 1533-1537, Dec. 1995.
- B. Zojer, B. Astegher, H. Jessner, R. Petschacher, “A 10 bit 75 MHz subranging A/D converter”, *IEEE Journal of Solid-State Circuits*, vol. 25, pp. 1339-1346, Dec. 1990.
- Y. Yoshi, M. Nakamura, K. Hirasawa, A. Kayanuma, K. Asano, “An 8 bit 350 MHz Flash ADC”, *ISSCC Digest of Technical Papers*, pp. 96-97, Feb. 1987.
- A. Dingwall, V. Zazzu, “An 8 MHz CMOS Subranging 8 bit A/D Converter”, *IEEE Journal of Solid-State Circuits*, vol. 20, pp. 1138-1143, Dec. 1985.



REFERENCES

- A. Cremonesi, F. Maloberti, G. Torelli, C. Vacchi, "An 8-bit Two-Step Flash A/D Converter for Video Applications", Proceedings of Custom Integrated Circuit Conference, pp. 6.3.1-6.3.4, May 1989.
- Bang-Sup Song, S. H. Lee, M. F. Tompsett, "A 10 bit 15 MHz Recycling Two Step A/D Converter", IEEE Journal of Solid-State Circuits, vol. 25, pp. 1328-1337, Dec. 1990.

Folding, Interpolating and Interleaved A/D Converters

- R. E. J. van de Grift, I. W. J. M. Rutten, M. van der Veen, "An 8 bit Video ADC Incorporating Folding and Interpolation Techniques", IEEE Journal of Solid-State Circuits, vol. 22, pp. 944-953, Dec. 1987.
- C. J. van Valburg, R. J. van de Plassche, "An 8 Bit 650 MHz Folding ADC", IEEE Journal of Solid-State Circuits, vol. 27, pp. 1662-1666, Dec. 1992.
- P. Vorenkamp, R. Roovers, "A 12 bit 60 MS/s Cascaded Folding and Interpolating ADC", IEEE Journal of Solid-State Circuits, vol. 32, pp. 1876-1886, Dec. 1997.
- A. G. W. Venes, R. van de Plassche, "An 80 MHz 80 mW 8 bit Folding A/D Converter with Distributed Track & Hold Preprocessing", IEEE Journal of Solid-State Circuits, vol. 31, pp. 1846-1853, Dec. 1996.



REFERENCES

- M. P. Flynn, D. J. Allstot, “CMOS Folding A/D Converters with Current-Mode Interpolation”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 1248-1257, Dec.1996.
- B. Nauta, A. G. W. Venes, “A 70 MS/s 110 mW 8-Bit CMOS Folding and Interpolating A/D Converter”, IEEE Journal of Solid-State Circuits, vol. 30, pp. 1302-1308, Dec. 1995.
- R. Roovers, “CMOS ADC 6bit 160 mW 3.3 V Interpolating Architecture”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 938-944, Dec. 1996.
- M. K. Mayers, “Time-Interleaved ADC 12 bit 1 MHz 25 mW Low Power Operation”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 169-178, Dec. 1996.
- W. C. Black Jr. and D. A. Hodges, “Time Interleaved Converter Arrays”, IEEE Journal of Solid-State Circuits, vol. 15, pp. 1022-1029, Dec. 1980.
- F. Goodenough, “Interpolators Put 10 bit 75 MHz A/D Converters in 8 bit Digital Process”, Electronic Design, pp. 29-30, Dec. 1989.
- M. Steyaert, R. Roovers, J. Craninckx, “A 100 MHz 8 bit CMOS Interpolating A/D Converter”, Proceedings of Custom Integrated Circuit Conference, pp 28.1.1-28.1.4, May 1993.



REFERENCES

Pipeline A/D Converters

- M. K. Mayers, S. W. Chin, “A 200 mW 1 MS/s 16 Bit Pipelined A/D Converter with On-Chip 32 Bit Microcontroller”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 1862-1872, Dec. 1996.
- P. C. Yu, H. Lee, “A 2.5 V 12 Bit 5 MS/s Pipelined CMOS ADC”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 1854-1861, Dec. 1996.
- T. Hsiung, K. Bacrania, R. Gokhale, “BiCMOS Fully-Differential Pipelined A/D Converter, 10 Bit 40 MS/s”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 1507-1510, Dec. 1996.
- D. W. Cline, “CMOS Pipelined A/D Converter, Power Optimized Design”, IEEE Journal of Solid-State Circuits, vol. 31, pp. 294-303, Dec. 1996.
- T. B. Cho, P. R. Gray, “A 10 Bit MS/s 35 mW Pipeline A/D Converter”, IEEE Journal of Solid-State Circuits, vol. 30, pp. 166-172, Dec. 1995.
- K. Nakamura, M. Hotta, L. R. Carley, D. J. Allstot, “An 85 mW 10 bit 40 MS/s CMOS Parallel Pipelined ADC”, IEEE Journal of Solid-State Circuits, vol. 30, pp. 173-183, Dec. 1995.



REFERENCES

- C. Yu, C. C. Chen, J. J. Cho, “CMOS Pipelined ADC Current Mode Circuit Technique”, IEEE Journal of Solid-State Circuits, vol. 30, pp. 522-532, Dec. 1995.
- W. T. Colleran, T. H. Phan, A. A. Abidi, “A 10 bit 100 MS/s Pipelined A/D Converter”, ISSCC Digest of Technical Papers, pp. 68-69, Feb. 1993.
- K. Kusumoto et al. “A 10 bit 20 MHz 30 mW Pipelined Interpolating CMOS ADC”, ISSCC Digest of Technical Papers, pp. 62-63, Feb. 1993.
- Y-M. Lin, B. Kim, P. R. Gray, “A 13 Bit 2.5 MHz Self-Calibrated Pipelined A/D Converter in 3 μ m CMOS”, IEEE Journal of Solid-State Circuits, vol. 26, pp. 628-636, Dec. 1991.
- K. W. Martin, “A High-Speed High-Accuracy Pipelined A/D Converter”, Proceedings of Asilomar Conference on Circuits, Systems and Computers, Nov. 1981.
- B. S. Song, M. F. Tompsett, K. R. Lakshmikumar, “A 12 bit 1 MS/s Capacitor Error-Averaging Pipelined A/D Converter”, IEEE Journal of Solid-State Circuits, vol. 23, pp. 1324-1333, Dec. 1988.
- P. Vorenkamp, J. P. M. Verdaasdonk, “A 10 Bit 50 MS/s Pipelined ADC”, ISSCC Digest of Technical Papers, pp. 32-33, Feb. 1992.



REFERENCES

- S. Sutarja, P. R. Gray, “A Pipelined 13 Bit 250 kS/s 5 V Analog-to-Digital Converter”, IEEE Journal of Solid-State Circuits, vol. 23, pp. 1316-1323, Dec. 1988.

Sigma Delta A/D Converters

- K. C. H. Chao, S. Nadeem, W. L. Lee, C. G. Sodini, “A Higher Order Topology for Interpolative Modulators for Oversampling A/D Converters”, IEEE Transactions of Circuits and Systems, vol. 37, pp. 309-318, Mar. 1990.
- V. F. Diaz, “A Design Environment for Switched Capacitor Noise Shaping A/D Converters”, Ph. D. Dissertation, University of Pavia, Department of Electronics, 1991.
- J. C. Candy, “A Use of Double Integration in Sigma-Delta Modulation”, IEEE Transactions on Communications, vol. 35, pp. 481-489, May 1987.
- F. Francesconi, G. Caiulo, V. Liberali, F. Maloberti, “A 30-mW 10.7-MHz Pseudo-N-Path Sigma-Delta Band-Pass Modulator”, Symposium on VLSI Circuits Digest of Technical Papers, pp. 60-61, June, 1996.
- F. Francesconi, V. Liberali, F. Maloberti, “A 10.7-MHz N-Path Fourth-Order Bandpass Sigma-Delta Modulator”, Proceedings of European Solid-State Circuit Conference, pp. 216-219, Sept. 1996.



REFERENCES

- S. R. Norsworthy, R. Schreier, G. C. Temes, “Delta-Sigma Data Converters: Theory, Design, and Simulation”, IEEE Press, New York, USA, 1997.
- M. J. Hawksford, “N-th Order Recursive Sigma-ADC Machinery at the Analogue-Digital Gateway”, Audio Engineering Society Convention, May 1985.
- Y. Matsuya, K. Uchimura, A. Iwata, T. Kobayashi, M. Ishikawa, T. Yoshitome, “A 16-Bit Oversampling A-to-D Conversion Technology Using Triple Integration Noise Shaping”, IEEE Journal of Solid-State Circuits, vol. 22, pp. 921-929, Dec. 1987.
- S. H. Ardalan, J. J. Paulos, “An Analysis of Nonlinear Behavior in Delta-Sigma Modulators”, IEEE Transactions on Circuits and Systems, vol. 34, pp. 593-603, June 1987.
- L. E. Larsen, T. Cataltepe, G. C. Temes, “Multi-Bit Oversampled $\Sigma\Delta$ A/D Converter with Digital Error Correction”, Electronic Letters, vol. 24, pp. 1051-1052, Aug. 1988.
- V. F. Dias, G. Palmisano, P. O’Leary, F. Maloberti, “Fundamental Limitations of Switched-Capacitor Sigma-Delta Modulators”, IEE Proceedings-G, vol. 139, Feb. 1992.
- D. A. Kerth, D. B. Kasha, T. G. Mellissinos, D. S. Piasecki, E. J. Swanson, “A 120 dB Linear Switched-Capacitor Delta-Sigma Modulator”, ISSCC Digest of Technical Papers, pp. 196-197, Feb. 1994.



REFERENCES

- R. W. Adams, T. W. Kwan, “Data-Directed Scrambler for Multi-bit Noise Shaping D/A Converters”, U.S. patent no. 5.404.142, Apr. 1995.
- R. T. Baird, T. S. Fiez, “Improved Delta-Sigma DAC Linearity Using Data-Weighted Averaging”, Proceedings of International Symposium on Circuits and Systems, pp. 13-16, May 1995.
- J. C. Candy, G. C. Themes, “Oversampling Methods for A/D and D/A Conversion”, Oversampling Delta-Sigma Data Converters, J. C. Candy and G. C. Themes, Ed., IEEE Press, New York, USA, 1992.
- F. Chen, B. H. Leung, “A High Resolution Multibit Sigma-Delta Modulator with Individual Level Averaging”, IEEE Journal of Solid-State Circuits, vol 30, pp. 430-460, Apr. 1995.
- V. F. Dias, V. Liberali, F. Maloberti, “TOSCA: a User-Friendly Behavioural Simulator for Oversampling A/D converters, Proceedings of International Symposium on Circuits and Systems, pp. 2677-2680, May 1991.

D/A Converters

- A. Cremonesi, F. Maloberti, G. Polito, “A 100 MHz CMOS DAC for Video-Graphic Systems”, IEEE Journal of Solid-State Circuits, vol. 24, pp. 635-639, June 1989.



REFERENCES

- A. Cremonesi, F. Maloberti, G. Torelli, C. Vacchi, "An 8-bit Two-Step Flash A/D Converter for Video Applications", Proceedings of Custom Integrated Circuit Conference, pp. 6.3.1-6.3.4, May 1989.
- S. Brigati, G. Caiulo, F. Maloberti, G. Torelli, "Active Compensation of Parasitic Capacitances for Very High Frequency CMOS DACs", Proceedings of International Symposium on Circuits and Systems, pp. 1208-1211, May 1993.
- D. W. J. Groeneveld, H. J. Schouwenaars, H. A. H. Termeer, C. A. A. Bastiaansen, "A Self Calibration Technique for Monolithic High Resolution D/A Converters", IEEE Journal of Solid-State Circuits, vol. 24, pp. 1571-1522, Dec. 1989.
- A. R. Hamade, "A Single-Chip All-MOS 8 Bit A/D Converter", IEEE Journal of Solid-State Circuits, vol.13, pp. 785-791, Dec. 1978.
- J. W. Yang, K. W. Martin, "High resolution Low-Power CMOS D/A Converter", IEEE Journal of Solid-State Circuits, vol. 24, pp. 1458-1461, Oct. 1989.
- H. J. Schouwenaars, D. W. J. Groeneveld, H. A. H. Termeer, "Low Power Stereo 16 Bit CMOS D/A Converter for Digital Audio", IEEE Journal of Solid-State Circuits, vol. 23, pp. 1290-1297, Dec. 1988.



REFERENCES

- P.H. Saul, J. S. Urquhart, “Techniques and Technology for High-Speed D/A Conversion”, IEEE Journal of Solid-State Circuits, vol. 19, pp. 628-68, Dec. 1984.

Other Techniques

- K. C. Hsieh, P. R. Gray, D. Senderowicz, “A Low Noise Chopper-Stabilized Differential Switched-Capacitor Filtering Fechnique”, IEEE Journal of Solid-State Circuits, vol. 16, pp. 708-715, Dec. 1981.
- P. W. Li, M. J. Chin, P. R. Gray, R. Castello, “A Ratio-Independent Algorithmic Analog-to Digital Conversion Technique”, IEEE Journal of Solid-State Circuits, vol.19, pp. 828-836, Dec. 1984.
- K. W. Martin, L. Ozcolak, Y. S. Lee, G. C. Themes, “A Differential Switched Capacitor Amplifier”, IEEE Journal of Solid-State Circuits, vol. 22 , pp. 104-106, Feb. 1987.
- A. Baschiroto, G. Brasca, F. Montecchi, F. Stefani, “Low Power BiCMOS SC Filter for Audio Codec Applications”, IEEE Journal of Solid-State Circuit, vol. 32, pp. 1127-1131, July 1997.

