

Exercise Circ07

Consider a CMOS fabrication process with the following process parameters:

$$k_n' = \mu_n C_{ox} = 120 \mu A/V^2, k_p' = \mu_p C_{ox} = 40 \mu A/V^2,$$

$$V_{th,n} = |V_{th,p}| = 0.6 V,$$

$L_{min} = 0.40 \mu m$ (minimum allowed channel length) for both N-channel and P-channel transistors,

$C_{ox} = 2 \text{ fF}/\mu m^2$ (gate capacitance per unit area),

$t_{ox} = 15 \text{ nm}$ (gate oxide thickness).

The used fabrication technology and the layout are such that, for each transistor, the drain capacitance and the source capacitance turn out to be equal to 20% and 25%, respectively, of the gate capacitance, whereas the overlap/fringing gate capacitance and the capacitances associated to interconnections are negligible.

Supply voltage V_{DD} is equal to 3 V.

The transistors in the elementary inverter used in an integrated circuit fabricated with the above process, have the following sizes:

N-channel transistor: channel width $W_n = 2.5 \mu m$; channel length $L_n = 0.4 \mu m$;

P-channel transistor: channel width $W_p = 7.5 \mu m$; channel length $L_p = 0.4 \mu m$.

As shown in Figure 1, a single inverter has to be included, as a buffer, between the above elementary inverter and a capacitive load C_L equal to 0.8 pF (which represents the input capacitance of a cascaded digital network).

 


Figure 1

The candidate is asked to design the buffer inverter so as adequately limit the overall delay time from node IN to node OUT.