

## Exercise Circ13

Consider a CMOS fabrication process with the following process parameters:

$$k_n' = \mu_n C_{ox} = 120 \mu A/V^2, \quad k_p' = \mu_p C_{ox} = 40 \mu A/V^2,$$

$$V_{th,n} = |V_{th,p}| = 0.6 \text{ V},$$

$L_{min} = 0.35 \mu m$  (minimum allowed channel length for both N-channel and P-channel transistors),

$C_{ox} = 2.5 \text{ fF}/\mu m^2$  (gate capacitance per unit area),

$t_{ox} = 12 \text{ nm}$  (gate oxide thickness).

Supply voltage  $V_{DD}$  is equal to 3 V.

The transistors in the elementary inverter used in the circuit shown in Figure 1, fabricated with the above process, have the following sizes:

N-channel transistors: channel width  $W_n = 3.5 \mu m$ ; channel length  $L_n = 0.35 \mu m$ ;

P-channel transistors: channel width  $W_p = 7 \mu m$ ; channel length  $L_p = 0.35 \mu m$ .

The used fabrication technology and the layout are such that, for each transistor, the drain capacitance and the source capacitance turn out to be equal to 20% and 25%, respectively, of the gate capacitance, whereas the overlap/fringing gate capacitance and the capacitances associated to interconnections are negligible.

By using the above elementary inverter, we implemented the circuit shown in figure 1, which is a ring oscillator where elementary inverters (equal to the above elementary inverter) are added to drive output lines. Capacitor  $C_L$ , which represents the load at node OUT, is equal to 0.8 pF.

The candidate is asked to:

- calculate the delay time of the elementary inverter in the circuit schematic in figure 1, justifying all the assumptions made, if any;
- estimate the oscillation frequency of the circuit in figure 1;
- calculate the rise time at node OUT and provide comments.

**Attention** - The following point d) is to be solved only provided that the above points a), b), and c) have been completely solved.

- Assume that the supply voltage  $V_{DD}$  can vary in the range from 2.7 V to 3.3 V and the threshold voltages  $V_{th,n}$  and  $|V_{th,p}|$  can vary in the range from 0.55 V and 0.65 V. The candidate is asked to calculate the minimum and the maximum oscillation frequency of the circuit in figure 1.

 


Figure 1